



CS-302 Digital Logic Design Update MCQS For Quiz-3 File Solve By Vu Topper RM



85 To 100% Marks



وَتَعَزُّ مِنْ تَشَاءٍ وَتَذُلُّ مِنْ تَشَاءٍ

PROFESSIONAL ONLINE ACADEMY



We Offers

LMS Handling

Important Notes

Online Classes

Assignments

Quiz & GDB's

Projects

**NOTHING
IS
IMPOSSIBLE**


**Join Us
Now**

For More Info

Contact us at:

Rizwan Manzoor

☎ **0322-4021365**

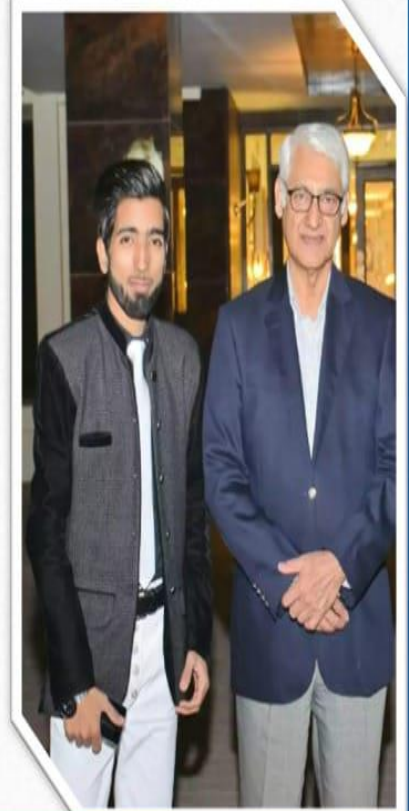

بري صحبت سے تنہائی بہتر ہے اور نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:1

(Marks:1)

Vu-Topper RM

Demultiplexer is also called _____

- A. Data router
- B. Data selector
- C. Data encoder

D. Data Distributor

Page 178

Question No:1

(Marks:1)

Vu-Topper RM

2-Input, 8-bit Multiplexer, by setting the S input to logic _____ the _____ inputs of both the multiplexers are selected.

- A. Low, B
- B. High, C
- C. High, B**
- D. Low, C

Question No:1

(Marks:1)

Vu-Topper RM

On a positive edge-triggered S-R flip-flop, the outputs reflect the input condition when _____

- A. The clock pulse is LOW
- B. The clock pulse is HIGH
- C. The clock pulse transition from HIGH to LOW

D. The clock pulse transition from LOW to HIGH

Google

Question No:1

(Marks:1)

Vu-Topper RM

A NOR based S-R latch is implemented using _____ gates instead of _____ gates.

- A. XOR, NAND
- B. NOR, XOR
- C. NOR, NAND**
- D. OR, XOR

Page 213

Question No:1

(Marks:1)

Vu-Topper RM

When the number 29 is represented on 7-segment display, which BCD input is represented on LSD display unit?

A. 1001

Page 172

بري صحبت سے تنهائي بهتر ہے اور تنهائي سے نيك صحبت بهتر ہے

For More Help Contact What's app 03224021365

- B. 1000
- C. 1100
- D. 1010

Question No:1

(Marks:1)

Vu-Topper RM

The GAL22V10 is a popular GAL device having _____ inputs and ten inputs/outputs.

A. 10

B. 12 **Page 194**

C. 14

D. 16

Question No:1

(Marks:1)

Vu-Topper RM

The operation of J-K flip-flop is similar to that of the SR flip-flop except that the J-K flip-flop _____

A. Doesn't have an invalid state **Page 232**

B. Sets to clear when both $J = 0$ and $K = 0$

C. It does not accept asynchronous inputs

D. It does not show transition on change in pulse

Question No:1

(Marks:1)

Vu-Topper RM

The counter states or the range of numbers of a counter is determined by the formula. ("n" represents the total number of flip-flops)

A. (n raise to power 2)

B. (n raise to power 2 and then minus 1)

C. (2 raise to power n)

D. (2 raise to power n and then minus 1)

Question No:1

(Marks:1)

Vu-Topper RM

We have a digital circuit. Different parts of circuit operate at different clock frequencies (4MHZ, 2MHZ and 1MHZ), but we have a single clock source having a fix clock frequency (4MHZ), to supply the

بری صحبت سے تہائی بہتر ہے اور تہائی سے نیک صحبت بہتر ہے

For More Help Contact What's app 03224021365

required frequency to each part of circuit, we can get help by using

A. J-K flip-flop

Page 257

B. J-d flip-flop

C. Both

D. None of the these

Question No:10

(Marks:1)

Vu-Topper RM

Tri-State Buffer is a _____ gate with a control line that disconnects the output from the input.

A. OR

B. AND

C. NOT

Page 196

D. NAND

Question No:10

(Marks:1)

Vu-Topper RM

GAL can be reprogrammed as instead of fuses E2CMOS logic is used which can be programmed to connect a _____ with a _____.

A. Column, row

Page 191

B. column, row

C. column, column

D. row, row

Question No:10

(Marks:1)

Vu-Topper RM

When the control line in tri-state buffer is high, the buffer operates like a _____ gate

A. NOT

Page 196

B. AND

C. OR

D. XOR

Question No:10

(Marks:1)

Vu-Topper RM

8-bit parallel data can be converted into serial data by using _____ multiplexer.

بري صحبت سے تنهائي بهتر ہے اور تنهائي سے نيك صحبت بهتر ہے

For More Help Contact What's app 03224021365

A. 8-to-1

Page 175

B. 8-to-4

C. 4-to-2

D. 4-to-4

Question No:10

(Marks:1)

Vu-Topper RM

In GAL16V8, each product term is implemented using a 32-bit input _____ gate.

A. OR

B. AND

Page 200

C. NOT

D. NAND

Question No:10

(Marks:1)

Vu-Topper RM

The declaration section of ABEL generally includes the device declaration, _____ declarations and set declarations.

A. Pin

Page 207

B. Cell

C. Model

D. System

Question No:10

(Marks:1)

Vu-Topper RM

System having memory elements are called _____ circuits.

A. Simplex

B. Sequential

Google

C. Quadrantal

D. Combinational

Question No:10

(Marks:1)

Vu-Topper RM

A standard interface for programming the In-System PLD consists of

A. 2 wire

B. 4 wire

Page 194

C. 8 wire

D. 16 wire

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:10

(Marks:1)

Vu-Topper RM

In gated SR latch, what is the value of the output if $EN=1$, $S=0$ and $R=1$?

A. 0

B. 1

C. 2

D. 3

Question No:10

(Marks:1)

Vu-Topper RM

An Astable multivibrator is known as a(n) _____

A. Oscillator

Page 258

B. Booster

C. One-shot

D. Dual-shot

Question No:20

(Marks:1)

Vu-Topper RM

In synchronous digital circuits the _____ of one flip-flop is connected to the _____ of a second flip-flop.

A. Input, Output

B. Output, input

Page 258

C. Input, clock signal

D. Clock signal, Output

Question No:20

(Marks:1)

Vu-Topper RM

A synchronous decade counter will have _____ flip-flops

A. 3

B. 4

Page 281

C. 7

D. 10

Question No:20

(Marks:1)

Vu-Topper RM

The _____ input overrides the _____ input

A. Asynchronous, synchronous

Page 369

B. Synchronous, asynchronous

C. Preset input (PRE), Clear input (CLR)

بري صحبت سے تنهائي بهتر ہے اور تنهائي سے نيك صحبت بهتر ہے

For More Help Contact What's app 03224021365

D. Clear input (CLR), Preset input (PRE)

Question No:20

(Marks:1)

Vu-Topper RM

To display the number ____ the BCD number 0010 representing the MSD is applied at the inputs of the BCD to 7-Segment display circuit connected to the MSD 7-Segment Display Digit.

A. 19

B. 29 **Page 172**

C. 39

D. 49

Question No:20

(Marks:1)

Vu-Topper RM

In 16-input multiplexer, the decoder inputs ____ and ____ enable one out of the four multiplexers.

A. C and D

Page 171

B. A and B

C. B and A

D. A and D

Question No:20

(Marks:1)

Vu-Topper RM

Flip flops are also called ____

A. Bi-stable multivibrators

Page 228

B. Bi-stable single vibrators

C. Bi-stable dual vibrators

D. Bi-stable transformer

Question No:20

(Marks:1)

Vu-Topper RM

Once the state diagram is drawn for any sequential circuit the next step is to draw

A. Transition table

B. Karnaugh map

C. Next- state table

D. Logic expression

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:20

(Marks:1)

Vu-Topper RM

_____ is said to occur when multiple internal variables change due to change in one input variable

- A. Hold delay
- B. Clock Skew

C. Race condition

Page 267

- D. Hold and Wait

Question No:20

(Marks:1)

Vu-Topper RM

In a 4-bit binary counter, the next state after the terminal count in the DOWN mode is _____

- A. 0001
- B. 0011
- C. 0000**
- D. 10000

Question No:20

(Marks:1)

Vu-Topper RM

The minimum time required for the input logic levels to remain stable before the clock transition occurs is known as the _____

A. Set-up time

Page 234

- B. Hold time
- C. Pulse Interval time
- D. Pulse Stability time (PST)

Question No:30

(Marks:1)

Vu-Topper RM

For a gated D-Latch if $EN=1$ and $D=1$ then $Q(t+1) =$ _____

- A. Invalid
- B. 1**
- C. 0
- D. $Q(t)$

Question No:30

(Marks:1)

Vu-Topper RM

A counter is implemented using three (3) flip-flops, possibly it will have _____ maximum output status.

- A. 2

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

B. 4

C. 8

Page 272

D. 10

Question No:30

(Marks:1)

Vu-Topper RM

The _____ output has the output of the OR gate connected through an XOR gate to the tri-state buffer.

A. PLA

B. Combinational

C. Combinational input/

D. Programmed Polarity

Page 18

Question No:30

(Marks:1)

Vu-Topper RM

The latch is said to be in logic _____ state when $Q=1$ and $Q'=0$ and it is in the logic low state when $Q=0$ and $Q'=1$.

A. Low

B. Zero

C. High

Page 211

D. Constant

Question No:30

(Marks:1)

Vu-Topper RM

The primary use of multiplexers is _____.

A. Data Router

B. Operation sequencing

C. Logic function generator

D. Parallel to Serial Converter

Page 172

Question No:30

(Marks:1)

Vu-Topper RM

If the S and R inputs of the gated S-R latch are connected together using a _____ gate then there is only a single input to the latch. The input is represented by D instead of S or R (A gated D-Latch)

A. OR

B. And

C. NOT

Page 226

D. XOR

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:30

(Marks:1)

Vu-Topper RM

In Complex mode of GAL16V8, OLMCs can be configured in _____ ways.

A. Two

Page 202

B. Fore

C. Five

D. Three

Question No:30

(Marks:1)

Vu-Topper RM

In 1-to-4 demultiplexer, how many select lines are required

A. 1 select lines

B. 2 select lines

Page 396

C. 3 select lines

D. 4 select lines

Question No:30

(Marks:1)

Vu-Topper RM

In case of cascading Integrated Circuit counters, the enable inputs and RCO of the Integrated Circuit counters allow cascading of multiple counters together

A. True

B. False

Question No:30

(Marks:1)

Vu-Topper RM

The PROM consists of a fixed non-programmable _____ Gate array configured as a decoder.

A. OR

B. AND

Page 182

C. XOR

D. NAND

Question No:40

(Marks:1)

Vu-Topper RM

The ____ enable input of the decoder when set to 1 disables the decoder and the multiplexers.

A. G

Page 171

B. B

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

- C. A
- D. S

Question No:40

(Marks:1)

Vu-Topper RM

If $S=1$ and $R=1$, for negative edge triggered flip-flop then

- A. Direct
- B. Invalid**
- C. Valid
- D. Indirect

Page 233

Question No:40

(Marks:1)

Vu-Topper RM

A decade counter can be implemented by truncating the counting sequence of a MOD-20 counter.

- A. True
- B. False**

Question No:40

(Marks:1)

Vu-Topper RM

Three cascaded modulus-10 counters have an overall modulus of.

- A. 30
- B. 100
- C. 1000**
- D. 10000

Question No:40

(Marks:1)

Vu-Topper RM

A-stable multi-vibrator continuously changes from one unstable state to the other without any_____.

- A. Output
- B. Variable
- C. Flip flop

D. External trigger

Page 258

Question No:40

(Marks:1)

Vu-Topper RM

The 74HC163 is a 4-bit Synchronous Counter.it has.....data output pins

- A. 2

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

B. 4 **Page 278**

C. 6

D. 8

Question No:40

(Marks:1)

Vu-Topper RM

A _____ attached to the Select inputs of the Demultiplexer routes the incoming serial bits to successive outputs where each bit is stored.

A. Data

B. Buffer

C. Memory

D. Counter **Page 178**

Question No:40

(Marks:1)

Vu-Topper RM

The OLMC can be configured to provide a feedback input signal to the AND gate array input. There are _____ possibilities.

A. Two

B. Five

C. Four

D. Three **Page 200**

Question No:40

(Marks:1)

Vu-Topper RM

The PLA can be programmed to give an output of constant ____ or ____.

A. 2.3

B. 0.1 **Page 190**

C. 0.0

D. 1.2

Question No:40

(Marks:1)

Vu-Topper RM

PLDs have In-System Programming (ISP) capability that allows the _____ to be programmed after they have been installed on a circuit board.

A. PALs

B. PLAs

C. PLDs **Page 194**

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

D. EPROM

Question No:50

(Marks:1)

Vu-Topper RM

Bi-stable devices remain in either of their _____ states unless the inputs force the device to switch its state Select correct option:

- A. Ten
- B. Eight
- C. Three

D. Two

Page 255

Question No:50

(Marks:1)

Vu-Topper RM

In Combinational Output with feedback to AND array, the active-state of the output is determined by the _____ input.

- A. OR
- B. NOT

C. XOR

Page 201

D. AND

Question No:50

(Marks:1)

Vu-Topper RM

Karnaugh map is used in designing

- A. a clock
- B. a counter
- C. an UP/DOWN counter

D. All of the above

Question No:50

(Marks:1)

Vu-Topper RM

The S-R latch has two inputs, therefore _____ different combinations of inputs can be applied to control the operation of the S-R latch.

A. Four

Page 212

B. Eight

C. Seven

D. Sixteen

Question No:50

(Marks:1)

Vu-Topper RM

بري صحبت سے تنهائي بهتر ہے اور تنهائي سے نيك صحبت بهتر ہے

For More Help Contact What's app 03224021365

A decade counter is _____

- A. Mod-3 counter
- B. Mod-5 counter
- C. Mod-8 counter

D. Mod-10 counter

Page 274

Question No:50

(Marks:1)

Vu-Topper RM

When the _____ Hz sampling interval is selected, the signal at the output of the J-K flip-flop has a time period of _____ seconds.

A. 1,2

B. 3,4

C. 5,6

D. 8,7

Question No:50

(Marks:1)

Vu-Topper RM

_____ is one of the examples of asynchronous inputs.

A. D input

B. J-K input

C. S-R input

D. Clear Input (CLR)

Page 235

Question No:50

(Marks:1)

Vu-Topper RM

The GAL16V8 has eight _____ each connected to eight product terms.

A. OLMCs

Page 200

B. POS

C. SOP

D. CELLS

Question No:50

(Marks:1)

Vu-Topper RM

_____ is used when the output is connected back to the input of the PAL or if the output pin is used as an input only.

A. Combinational Input/Output

Page 185

B. Combinational Input/Output

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

- C. Combinational Output
- D. Programmable polarity

Question No:50

(Marks:1)

Vu-Topper RM

The next state table for REQ1, FLOOR1 and OPEN inputs indicates that the _____ can be pressed at any time either on the first floor or the second floor in elevator.

- A. REQ0
- B. OPEN
- C. REQ1**
- D. FLOOR1

Page 370

Question No:60

(Marks:1)

Vu-Topper RM

_____ Yellow signal controlling the traffic on the East-West section.

- A. EWYel**
- B. NSRed
- C. EWRed
- D. TMRST

Page 375

Question No:60

(Marks:1)

Vu-Topper RM

An 8-bit converter requires _____ weighted resistors which have exact values otherwise the output of the converter is not accurate.

- A. Seven
- B. Ten
- C. Eight**
- D. Nine

Page 451

Question No:60

(Marks:1)

Vu-Topper RM

ROMs and PROMs retains information _____ even if the supply voltage is removed.

- A. Two days

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

B. Four days

C. Permanently

Page 417

D. Ten days

Question No:60

(Marks:1)

Vu-Topper RM

Two states are said to be equal if they have exactly same_____.

A. Output

B. Input

Page 325

C. Both

D. None

Question No:60

(Marks:1)

Vu-Topper RM

To implement the counter using S-R flip-flops instead of J-K flip-flops, the _____ transition table is used.

A. S-R

Page 316

B. D-R

C. J-K

D. None

Question No:60

(Marks:1)

Vu-Topper RM

FLASH memory cell is implemented using a single floating-gate_____transistor.

A. POS

B. MOS

Page 412

C. LOS

D. GOS

Question No:60

(Marks:1)

Vu-Topper RM

Two State variables allow a maximum of _____ states.

A. Two

بري صحبت سے تنهائي بهتر ہے اور تنهائي سے نيك صحبت بهتر ہے

For More Help Contact What's app 03224021365

B. Four

Page 385

C. Six

D. Eight

Question No:60

(Marks:1)

Vu-Topper RM

There are ____ type of EPROM

A. One

B. Two

Page 411

C. Three

D. Four

Question No:60

(Marks:1)

Vu-Topper RM

Synchronous SRAM uses a clock signal which is used by the _____ to synchronize its activities.

A. ALU

B. Control Unit

C. Address Bus

D. Microprocessor

Page 398

Question No:60

(Marks:1)

Vu-Topper RM

Analogue signals are converted into Digital signals by _____ converters.

A. Analogue to Analogue (A/A)

B. Analogue to Digital (A/D)

Page 434

C. Digital to Analogue (D/A)

D. Digital to Digital (D/D)

Question No:70

(Marks:1)

Vu-Topper RM

The duration for which the elevator doors are opened, and remain open,

برى صحبت سے تنہائی بہتر ہے اور تنہائی سے نیک صحبت بہتر ہے

For More Help Contact What's app 03224021365

and time it takes for the elevator to move from one floor to the next can be determined by a/an_____.

A. Input signal

B. Clock signal

Page 365

C. Output signal

D. None

Question No:70

(Marks:1)

Vu-Topper RM

Memories are implemented in_____bit data unit sizes

A. 1,2 and 6

B. 1,4 and 8

Page 425

C. 2,3 and 6

D. 4,4 and 8

Question No:70

(Marks:1)

Vu-Topper RM

PALs tend to execute _____ logic.

A. SPD

B. SOP

C. SAC

D. SAP

Question No:70

(Marks:1)

Vu-Topper RM

There are _____ possible combinations of the Simple Mode in which OLMC can be configured.

A. Three

Page 201

B. Four

C. Five

D. Six

بري صحبت سے تنهائي بهتر ہے اور تنهائي سے نيك صحبت بهتر ہے

For More Help Contact What's app 03224021365

Question No:70

(Marks:1)

Vu-Topper RM

If $S=1$ and $R=0$, then for positive edge triggered flip-flop $Q(t+1) = \underline{\hspace{2cm}}$

A. 0

B. 1 **Page 230**

C. Invalid

D. Input is invalid

Question No:70

(Marks:1)

Vu-Topper RM

According to Moore circuit, the output of synchronous sequential circuit depend/s on _____ of flip flop.

A. Previous state

B. Present state

C. Next state

D. External state

Question No:70

(Marks:1)

Vu-Topper RM

The outputs of SR latches in elevator state machine are feed back to the _____ gate array for connection to the D-flipflops.

A. NOT

B. AND

Page 372

C. OR

D. XOR

Question No:70

(Marks:1)

Vu-Topper RM

In memory write cycle, the time for which the WE signal remains active is known as the _____.

A. Write address setup

B. Write pulse width

Page 397

C. Write delay width

D. Write data time

بري صحبت سے تڻهائي بهتر هے اور تڻهائي سے نيڪ صحبت بهتر هے

For More Help Contact What's app 03224021365

Question No:70

(Marks:1)

Vu-Topper RM

_____ is one of the examples of synchronous inputs.

A. J-K input

Page 235

B. EN input

C. Preset input (PRE)

D. Clear Input (CL)

Question No:70

(Marks:1)

Vu-Topper RM

_____ occurs when the same clock signal arrives at different times at different clock inputs due to propagation delay.

A. Race condition

B. Clock Skew

Page 226

C. Ripple Effect

D. None of given options

Question No:80

(Marks:1)

Vu-Topper RM

A latch is a temporary storage device that has _____ stable states.

A. Two

Page 211

B. Three

C. Four

D. Five

Question No:80

(Marks:1)

Vu-Topper RM

RCO stands for _____

A. Reconfiguration Counter Output

B. Ripple Counter Output

C. Reconfiguration Clock Output

D. Ripple Clock Output

Page 285

Question No:80

(Marks:1)

Vu-Topper RM

A Divide-by-20 counter can be achieved by using

A. Flip-Flop and DIV 10

B. Flip-Flop and DIV 16

C. Flip-Flop and DIV 32

D. Div 10 and DIV 16

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:80

(Marks:1)

Vu-Topper RM

The terminal count of a modulus-13 binary counter is

A. 0000

B. 1111

C. 1101

D. 1100

Question No:80

(Marks:1)

Vu-Topper RM

Divide-by-32 counter can be achieved by using-----

A. Flip-Flop and DIV 10

B. Flip-Flop and DIV 16

C. Flip-Flop and DIV 32

D. DIV 16 and DIV 32

Question No:80

(Marks:1)

Vu-Topper RM

A 4-bit binary UP/DOWN counter is in the binary state zero. the next state in the DOWN mode is_____

A. 1111

B. 1110

C. 0001

D. 1000

Question No:80

(Marks:1)

Vu-Topper RM

Flash memory Operation are classified into _____ different operation.

A. One

B. Two

C. Three

D. Four

Page 413

Question No:80

(Marks:1)

Vu-Topper RM

In designing any counter, the transition from a current state to the next state is determined by-----

A. Current state and inputs

Page 332

B. Only inputs Only current state

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

- C. Positive-Edge triggered
- D. Negative-Edge triggered

Question No:80

(Marks:1)

Vu-Topper RM

A negative edge-triggered flip-flop changes its state when

Enable input (EN) is set

- A. Preset input (PRE) is set
- B. Enable input (EN) is set
- C. Low-to-high transition of clock
- D. High-to-low transition of clock**

Page 228

Question No:80

(Marks:1)

Vu-Topper RM

In distributed mode, for a 1024 x 1024 DRAM memory and a refresh cycle of 8 msec, each of the 1024 rows has to be refreshed in ____when Distributed refresh is used.

- A. 4.8 microsec
- B. 5.9 microsec
- C. 7.8 microsec**
- D. 5.5 microsec

Page 406

Question No:90

(Marks:1)

Vu-Topper RM

The 64-cell array organized as 8 x 8 cell array is considered as a 64-byte memory

- A. as a 16 byte memory
- B. as an 8 byte memory**
- C. as an 4 byte memory
- D. None of the given

Page 387

Question No:90

(Marks:1)

Vu-Topper RM

____ Counters as the name indicates are not triggered simultaneously

- A. Asynchronous**
- B. Synchronous
- C. Positive-Edge triggered

Page 262

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

D. Negative-Edge triggered

Question No:90

(Marks:1)

Vu-Topper RM

You have to choose suitable option when your timer will reset by considering this given code:

TRSTATE.CLK = clk;

TMRST: = (TRSTATE == NSY2) # (TRSTATE == EWY2);

A. NSY2 or EWY2

B. NSSR or TMRST

C. EWSR or NSRED

D. EWRed or EWYel

Question No:90

(Marks:1)

Vu-Topper RM

Which of the following is a volatile memory?

A. DRAM

B. PROM

C. EPROM

D. EEPROM

Question No:90

(Marks:1)

Vu-Topper RM

The counter states or the range of the number of a counter is determined by the formula("n" represented the total number of flip-flops)

A. 2 raise to power n

B. (n raise to power 2)

C. (n raise to power 2 and then minus 1)

D. (2 raise to power n and then minus 1)

Question No:90

(Marks:1)

Vu-Topper RM

In DRAM read cycle R /W- signal is activated to read data which is made available on the _____ data line.

A. D(IN)

B. D(OUT)

C. D(AB)

D. D(INT)

Page 405

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:90

(Marks:1)

Vu-Topper RM

A SOP expression can be implemented by an _____ combination of gates.

A. AND-OR

Page 78

B. OR-XOR

C. AND-NAND

D. XOR-NOR

Question No:90

(Marks:1)

Vu-Topper RM

A 3-variable Karnaugh map has

A. Eight cells

Page 89

B. three cells

C. sixteen cells

D. four cells

Question No:90

(Marks:1)

Vu-Topper RM

The ABEL Input file can use a _____ instead of the equation to specify the Boolean expressions.

A. Truth Table

Page 370

B. Logic Circuit

C. State Diagram

D. Karnaugh Map

Question No:90

(Marks:1)

Vu-Topper RM

In the keyboard encoder, how many times per second does the ring counter scan the key board?

A. 650 scans/second

B. 600 scans/second

C. 625 scans/second

D. 700 scans/second

Question No:100

(Marks:1)

Vu-Topper RM

In NAND based S-R latch, output of each _____ gate is connected to the input of the other _____ gate.

A. NAND, NAND

Page 211

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

- B. NOR, NAND
- C. NAND, NOR
- D. NOR, NOR

Question No:55

(Marks:1)

Vu-Topper RM

Select the mode of programming in which GAL16V8 can be programmed:

- A. All of the given**
- B. Simple Mode
- C. Complex Mode
- D. Registered Mode

Question No:56

(Marks:1)

Vu-Topper RM

Consider the sum of weight method for converting decimal into binary value, _____ is the highest weight for 411.

- A. 256**
- B. 257
- C. 258
- D. 259

Question No:58

(Marks:1)

Vu-Topper RM

The Transition table is very similar to the _____ table.

- A. State** **Page 382**
- B. Truth
- C. State
- D. Transition

Question No:59

(Marks:1)

Vu-Topper RM

Two types of memories namely the first in-first out (FIFO) memory and last in first out (LIFO) are implemented using _____.

- A. Shift Registers** **Page 417**
- B. Circular Buffers
- C. Ring Buffers
- D. Reduce Registers

بري صحبت سے تتهائي بهتر هے اور تتهائي سے نيك صحبت بهتر هے

For More Help Contact What's app 03224021365

Question No:60

(Marks:1)

Vu-Topper RM

For a down counter that counts from (111 to 000), if current state is "101" the next state will be _____.

A. 110

B. 101

C. 100

D. 001

Question No:61

(Marks:1)

Vu-Topper RM

The NOR logic gate is the same as the operation of the _____ gate with an inverter connected to the output.

A. NAND

B. AND

C. OR

D. NOT

Question No:62

(Marks:1)

Vu-Topper RM

The ROM used by a computer is relatively _____ as it stores few bytes of code used to Boot the Computer system on power up.

A. Small

Page 423

B. Heavy

C. High

D. Normal

Question No:63

(Marks:1)

Vu-Topper RM

Cin is part of _____ Adder.

A. Full

B. Half

C. Single

D. Double

Question No:64

(Marks:1)

Vu-Topper RM

Which one flip-flop has an invalid output state?

A. SR

B. T

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

- C. JK
- D. DK

Question No:65

(Marks:1)

Vu-Topper RM

The maximum value, represented by a single hexadecimal digit is ____.

- A. "F"**
- B. "E"
- C. "G"
- D. "H"

Question No:66

(Marks:1)

Vu-Topper RM

As data values are written or read from the RAM Stack Pointer Register increments or decrements its contents always pointing to the stack ____.

- A. Top**
- B. Bottom
- C. Down
- D. Vertex

Page 422

Question No:68

(Marks:1)

Vu-Topper RM

Adding two octal numbers "36" and "71" result in _____.

- A. 127**
- B. 213
- C. 123
- D. 345

Question No:69

(Marks:1)

Vu-Topper RM

The Static Ram (SRAM) is non-volatile and is not a _____ density memory as a latch is required to store a single bit of information.

- A. High**
- B. Low
- C. Medium
- D. Hot

Page 417

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:70

(Marks:1)

Vu-Topper RM

If two numbers in BCD representation generate an invalid BCD number then the binary _____ is added to the result.

A. 1001

B. 1000

C. 1111

D. 0011

Question No:71

(Marks:1)

Vu-Topper RM

A multiplexer with a register circuit converts

A. Parallel data to serial **Page 356**

B. Serial data to parallel

C. Serial data to serial

D. Parallel data to parallel

Question No:72

(Marks:1)

Vu-Topper RM

Implementation of Latch is required almost _____ transistor.

A. Six

Page 417

B. Two

C. Three

D. Four

Question No:73

(Marks:1)

Vu-Topper RM

The Synchronous SRAM also has a Burst feature which allows the Synchronous SRAM to read or write up to _____ location(s) using a single address.

A. One

B. Two

C. Three

D. Four

Page 399

Question No:75

(Marks:1)

Vu-Topper RM

The Test Vector definition defines the test vectors for all the three counter inputs and _____ counter output/outputs.

A. Three

Page 362

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

- B. Four
- C. Five
- D. One

Question No:76

(Marks:1)

Vu-Topper RM

Subtractors also have output to check if 1 has been _____.

A. Primed

- B. Shifted
- C. Complemented
- D. Borrowed

Question No:77

(Marks:1)

Vu-Topper RM

The terminal count of a 4-bit binary counter in the DOWN mode is _____

A. 0000

- B. 0011
- C. 1100
- D. 1111

Question No:78

(Marks:1)

Vu-Topper RM

The power consumed by a flip-flop is defined by _

A. $P = V_{cc} \times I_{cc}$

Page 235

- B. $P = I_{cc} \times R_{cc}$
- C. $P = V_{cc} \times R_{cc}$
- D. $P = M_{cc} \times V_{cc}$

Question No:79

(Marks:1)

Vu-Topper RM

The low to high or high to low transition of the clock is considered to be a(n) _____

A. Edge

Page 228

- B. Add
- C. Odd
- D. Out

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:81

(Marks:1)

Vu-Topper RM

A flip-flop is connected to +5 volts and it draws 5 mA of current during its operation, the power dissipation of the flip-flop is

A. 25 mW

Page 242

B. 10 mW

C. 64 mW

D. 1024 mW

Question No:82

(Marks:1)

Vu-Topper RM

The diagram above shows the general implementation of _____ form

A. POS

Page 122

B. COS

C. GOS

D. FOS

Question No:83

(Marks:1)

Vu-Topper RM

If the voltage drop across the active load is 0 volts due to absence of current the comparator output is a _____.

A. 0

B. 1

Page 417

C. 2

D. 3

Question No:84

(Marks:1)

Vu-Topper RM

A 4- bit UP/DOWN counter is in DOWN mode and in the 1010 state. on the next clock pulse, to what state does the counter go?

A. 1001

B. 1011

C. 0011

D. 1100

Question No:86

(Marks:1)

Vu-Topper RM

In designing any synchronous counter a modulus number is used which determine the number of..... used in a counter.....

A. Registers

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

B. Flip Flops

C. Counters

D. Latches

Question No:87

(Marks:1)

Vu-Topper RM

A positive edge-triggered flip-flop changes its state when

A. Preset input (PRE) is set

B. Enable input (EN) is set

C. High-to-low transition of clock

D. Low-to-high transition of clock

Page 221

Question No:88

(Marks:1)

Vu-Topper RM

The asynchronous inputs are normally labeled _____ and _____, and are normally active _____ inputs.

A. PRE, CLR, LOW

B. ON, OFF, HIGH

C. START, STOP, LOW

D. SET, RESET, HIGH

Question No:89

(Marks:1)

Vu-Topper RM

Assume a J-K flip-flop has 1s on the J and K inputs. The next clock pulse will cause the output to _____.

A. set

B. reset

C. latch

D. Toggle

Question No:90

(Marks:1)

Vu-Topper RM

In synchronous systems, the exact times at which any output can change state are determined by a signal commonly called the _____.

A. traffic

B. D

C. flip-flop

D. Clock

بري صحبت سے تھائی بہتر ہے اور تھائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:91

(Marks:1)

Vu-Topper RM

Which is not an example of a truncated modulus?

A. 8

B. 9

C. 11

D. 15

Question No:93

(Marks:1)

Vu-Topper RM

A Nibble consists of _____ bits

A. 4

Page 394

B. 6

C. 8

D. 10

Question No:94

(Marks:1)

Vu-Topper RM

_____ flip-flops are obsolete now.

A. Edge-triggered

B. Master-Slave

Page 257

C. T-Flipflop

D. D-Flipflop

Question No:96

(Marks:1)

Vu-Topper RM

When an eight bit serial in/serial out shift register is used for a 24 micro seconds time delay, the clock frequency must be Select correct option:

A. 41.67 KHz

B. 333 KHz

C. 125 KHz

D. 8 MHz

Question No:97

(Marks:1)

Vu-Topper RM

The 74HC163 is a 4-bit Synchronous Counter. it has.....parallel data inputs pins

A. 2

B. 4

Page 278

C. 6

بري صحبت سے تنهائي بهتر ہے اور تنهائي سے نيك صحبت بهتر ہے

For More Help Contact What's app 03224021365

D. 8

Question No:99

(Marks:1)

Vu-Topper RM

Divide-by-160 counter is achieved by using

- A. Flip-Flop and DIV 10
- B. Flip-Flop and DIV 16
- C. DIV 16 and DIV 32
- D. DIV 16 and DIV 10**

Question No:100

(Marks:1)

Vu-Topper RM

A 4-bit binary up/down counter is in the binary state of zero. The next state in the UP mode is:

- A. 1111**
- B. 1110
- C. 0001
- D. 1000

Question No:101

(Marks:1)

Vu-Topper RM

A divide-by-10 ring counter requires a minimum of

- A. Twelve flip-flops
- B. Four flip-flops
- C. Ten flip-flops**
- D. Five flip-flops

Google

Question No:102

(Marks:1)

Vu-Topper RM

A 32-bit data word consists of:

- A. 2 Byte
- B. 4 Byte**
- C. 6 Byte
- D. 8 Byte

Google

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:103

(Marks:1)

Vu-Topper RM

Which of the following memories uses one transistor and one capacitor as basic memory unit?

- A. ROM
- B. PROM
- C. RAM
- D. DRAM**

Google

Question No:105

(Marks:1)

Vu-Topper RM

Each stage of Master-slave flip-flop works at _____ of the clock signal

- A. One half**
- B. Full
- C. Center
- D. None

Question No:106

(Marks:1)

Vu-Topper RM

In memory read cycle, the read cycle is initiated by

- A. Applying the address signals**
- B. Digital
- C. Analog
- D. None

Page 397

Question No:107

(Marks:1)

Vu-Topper RM

The chip enable access time which is the time for the valid data to appear after the _____ transition of the chip select signal $\overline{CS}$.

- A. High-to-low**
- B. Low -to-high
- C. High
- D. Low

Page 397

بري صحبت سے تھائی بہتر ہے اور تھائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:108

(Marks:1)

Vu-Topper RM

The FAST Model Page Access allows _____ memory read and access times when reading successive data values stored in consecutive locations on the same row.

A. Faster

Page 406

B. Slow

C. High

D. None

Question No:109

(Marks:1)

Vu-Topper RM

A modulus-14 counter has fourteen states requiring

A. 4 flip flops

B. 6 flip flops

C. 8 flip flops

D. 2 flip flops

Question No:110

(Marks:1)

Vu-Topper RM

A memory organized to store nibble data values requires a _____ wide data bus.

A. 4-bit

Page 390

B. 2

C. 3

D. 1

Question No:111

(Marks:1)

Vu-Topper RM

If the number of samples that are collected is reduced by half, the reconstructed signal will be _____ from/to the original.

A. Very different

Page 1

B. Simple

C. Slow

D. Difficult

Question No:112

(Marks:1)

Vu-Topper RM

A 8-bit serial in / parallel out shift register contains the value "8", clock

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

signal(s) will be required to shift the value completely out of the register.

A. 8

Page 356

B. 6

C. 4

D. 2

Question No:113

(Marks:1)

Vu-Topper RM

The terminal count of a modulus -13 binary counter is

A. 1101

B. 1111

C. 0000

D. 1100

Question No:114

(Marks:1)

Vu-Topper RM

THE FOUR OUTPUTS OF TWO 4-INPUT MULTIPLEXERS, CONNECTED TO FORM A 16-INPUT MULTIPLEXER, ARE CONNECTED TOGETHER THROUGH A 4-INPUT _____

A. NOT

B. XOR

C. GATE

D. OR

Page 171

Question No:115

(Marks:1)

Vu-Topper RM

Number of states in an 8-bit Johnson counter sequence are:

A. 12

B. 8

Page 347

C. 4

D. 16

Question No:117

(Marks:1)

Vu-Topper RM

Consider A=1, B=0, C=1. A, B and C represent the input of three-bit NAND gate, the output of the NAND gate will be _____.

A. One

Page 46

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

- B. Two
- C. Three
- D. Four

Question No:118

(Marks:1)

Vu-Topper RM

The 74HC163 is a 4-bit Synchronous counter, it has _____ data output pins.

A. 4 **Page 278**

- B. 6
- C. 2
- D. 8

Question No:119

(Marks:1)

Vu-Topper RM

For a Standard SOP expression, a _____ is placed in the cell corresponding to the product term (Minter) present in the expression.

A. 1 **Page 90**

- B. 2
- C. 3
- D. 4

Question No:120

(Marks:1)

Vu-Topper RM

Two signals _____ and _____ provide the timing inputs to the State Machine.

A. LTIME and STIME **Page 374**

- B. NSSR and EWSR
- C. LTIME and STIME
- D. PTIME and QTIM

Question No:121

(Marks:1)

Vu-Topper RM

Which signal must remain valid in memory write cycle after data is applied at the data input lines and must remain valid for a minimum time duration t_{WD} ?

A. $\overline{WE}$ **Page 397**

- B. CS

بري صحبت سے تھائی بہتر ہے اور تھائی سے نیک صحبت بہتر ہے

For More Help Contact What's app 03224021365

- C. VS
- D. OE

Question No:122 (Marks:1) **Vu-Topper RM**

Implementation of the FIFO buffer in _____ is usually takes the form of a circular buffer.

- A. RAM** **Page 420**
- B. ROM
- C. Both
- D. None

Question No:123 (Marks:1) **Vu-Topper RM**

The output of a NAND gate is _____ when all the inputs are one.

- A. Zero** **Page 47**
- B. One
- C. Available
- D. Not available

Question No:124 (Marks:1) **Vu-Topper RM**

Implementing the Adjacent 1s detector circuit directly from the function table based on the SOP form requires _____ gates for the 8 product terms (minterms) with an 8-input OR gate.

- A. 8 AND**
- B. 8 OR
- C. 8 NOT
- D. 8 XOR

Question No:125 (Marks:1) **Vu-Topper RM**

In Master-Slave flip-flop the Clock signal is connected to Slave flip-flop using _____ gate

- A. NOT**
- B. OR
- C. AND
- D. XOR

بري صحبت سے تھائی بہتر ہے اور تھائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:127

(Marks:1)

Vu-Topper RM

Smallest unit of binary data is a _____

A. Bit

Page 387

B. Byte

C. Char

D. None

Question No:128

(Marks:1)

Vu-Topper RM

To parallel load a byte of data into a shift register, there must be

A. One clock pulse

B. Two clock pulse

C. Three clock pulse

D. Four clock pulse

Question No:129

(Marks:1)

Vu-Topper RM

Stack is an acronym for _____

A. LIFO memory

Page 429

B. FIFO memory

C. Both

D. None

Question No:130

(Marks:1)

Vu-Topper RM

The 4-bit 2's complement representation of "+5" is _____

A. 0101

B. 1010

C. 0011

D. 1000

Question No:131

(Marks:1)

Vu-Topper RM

The OR gate performs Boolean _____.

A. Addition

Page 42

B. Old

C. Multiply

D. Sub

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:132

(Marks:1)

Vu-Topper RM

In _____ Q output of the last flip-flop of the shift register is connected to the data input of the first flipflop of the shift register.

A. Ring counter

Page 355

B. Star counter

C. Bus counter

D. System counter

Question No:134

(Marks:1)

Vu-Topper RM

Following Is the circuit diagram of mono-stable device which gate will be replaced by the red colored rectangle in the circuit.

A. XNOR

Page 262

B. NOT

C. OR

D. AND

Question No:135

(Marks:1)

Vu-Topper RM

With a 100 KHz clock frequency, eight bits can be serially entered into a shift register in

A. 80 micro seconds

B. 20 micro seconds

C. 40 micro seconds

D. 60 micro seconds

Question No:136

(Marks:1)

Vu-Topper RM

The design and implementation of synchronous counters start from ____.

A. State diagram

Page 319

B. level diagram

C. Both

D. None of the these

Question No:137

(Marks:1)

Vu-Topper RM

In Synchronous systems, the output of all the digital circuits changes when an enable signal is applied instead of the clock signal.

بري صحبت سے تھائی بہتر ہے اور تھائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

A. True
B. False

Page 228

Question No:138 (Marks:1) **Vu-Topper RM**

The glitches due to "Race Condition" can be avoided by using a _____

A. Negative-Edge triggered flipflops **Page 260**

- B. Positive -Edge triggered flipflops
- C. Gated flip-flops
- D. Pulse triggered flip-flops

Question No:139 (Marks:1) **Vu-Topper RM**

A mono-stable device only has a single stable state-----

A. True **Page 262**

B. False

Question No:142 (Marks:1) **Vu-Topper RM**

When an Op-Amp is used as an inverting amplifier, the input signal is applied at its Inverted input through a _____resistance.

A. Parallel

B. Series **Page 439**

Question No:143 (Marks:1) **Vu-Topper RM**

In asynchronous digital systems all the circuits change their state with respect to a common clock

A. False **Page 245**

B. True

Question No:144 (Marks:1) **Vu-Topper RM**

State of flip-flop can be switched by changing its

A. Input signal

- B. Output signal
- C. Momentary Signal
- D. Contemporary Signal

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:145

(Marks:1)

Vu-Topper RM

3-to-8 decoder can be used to implement Standard SOP and POS Boolean expressions

A. True

Page 161

B. False

Question No:146

(Marks:1)

Vu-Topper RM

Memory is arranged in _____.

A. Two-dimensional manner

Page 396

B. linear fashion

Question No:147

(Marks:1)

Vu-Topper RM

A FIELD-PROGRAMMABLE LOGIC ARRAY CAN BE PROGRAMMED BY THE USER AND NOT BY THE MANUFACTURER.

A. True

Page 182

B. False

Question No:148

(Marks:1)

Vu-Topper RM

A _____ can not operate without a memory element.

A. Counter

Page 211

B. Register

Question No:150

(Marks:1)

Vu-Topper RM

A complete unit of information is sometimes called a _____.

A. Word

Page 387

B. Byte

Question No:151

(Marks:1)

Vu-Topper RM

If a circuit suffers "Clock Skew " problem, the output of circuit can't be guaranteed.

A. True

B. False

بري صحبت سے تھائی بہتر ہے اور تھائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:152

(Marks:1)

Vu-Topper RM

The combinational digital circuits have _____ storage element; therefore, combinational circuits handle only instantaneous inputs.

A. No

Page 210

B. Yes

Question No:153

(Marks:1)

Vu-Topper RM

Following is standard POS expression

A. True

B. False

Question No:154

(Marks:1)

Vu-Topper RM

The inputs can be directly mapped to Karnaugh maps.

A. J-K

Page 300

B. S-R

C. External

D. Flip-flop

Question No:155

(Marks:1)

Vu-Topper RM

The synchronous counters are also known as Ripple Counters:

A. True

B. False

Question No:156

(Marks:1)

Vu-Topper RM

To write data to the memory the memory the write cycle is initiated by

A. Applying the address signals

Page 397

B. Applying the digital address

Question No:157

(Marks:1)

Vu-Topper RM

The minimum time for which the input signal has to be maintained at the input of flip-flop is called _____ of the flip-flop.

Hold time

Page 242

بري صحبت سے تنهائي بهتر ہے اور تنهائي سے نيك صحبت بهتر ہے

For More Help Contact What's app 03224021365

Question No:158

(Marks:1)

Vu-Topper RM

A-stable multi-vibrator is an Oscillator which does not have any____

Astable Multivibrator

Google

Question No:159

(Marks:1)

Vu-Topper RM

The normal data inputs to a flip-flop (D, S and R, J and K, T) are referred to as ____ inputs.

Synchronous

Question No:160

(Marks:1)

Vu-Topper RM

UVEPROM is stands for-----

Ultra-Violet Erasable Programmable Read Only Memory.

Question No:161

(Marks:1)

Vu-Topper RM

-----are implemented by combining combinational circuits with memory elements.

A. PLA

B. PLDS

C. System

D. Sequential circuits

Page 211

Question No:162

(Marks:1)

Vu-Topper RM

The EPROM uses____array with an isolated-gate structure.

NMOSFET Page 411

Question No:163

(Marks:1)

Vu-Topper RM

A one-shot mono-stable device contains _

NOR gate, Resistor, Capacitor and NOT Gate

Question No:164

(Marks:1)

Vu-Topper RM

In sequential circuits memory elements are connected with_____.

Common clock

بري صحبت سے تنهائي بهتر ہے اور تنهائي سے نيک صحبت بهتر ہے

For More Help Contact What's app 03224021365

Question No:165

(Marks:1)

Vu-Topper RM

The alternate solution for a multiplexer and a register circuit is ____.

Parallel in / Serial out shift register Page356

Question No:166

(Marks:1)

Vu-Topper RM

Which of the following output equations determines the output of the state machine?

Max-Q0Q1EN

Page 382

Question No:167

(Marks:1)

Vu-Topper RM

The CONSTATE.CLK = Clock is used to indicate that the _____ state variables change on a clock transition.

CONSTATE

Question No:168

(Marks:1)

Vu-Topper RM

The n flip-flops store _____ states.

2^n

Question No:169

(Marks:1)

Vu-Topper RM

Why demultiplexer is called a data distributor?

Single input to Single Output

Question No:170

(Marks:1)

Vu-Topper RM

The AND Gate performs a logical _____ function.

Multiplication

Page 40

Question No:171

(Marks:1)

Vu-Topper RM

The _____ gate and _____ gate implementation connected at the B input of the 4-bit Adder is used to allow Complemented or Un-Complemented B input to be connected to the Adder input.

AND,OR

Page 146

بري صحبت سے تھائی بہتر ہے اور تھائی سے نیک صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:172

(Marks:1)

Vu-Topper RM

The domain of the expression $AB'CD + AB' + C'D + B$ is

A, B, C and D

Question No:173

(Marks:1)

Vu-Topper RM

When the transmission line is idle in an asynchronous transmission

A. It is set to logic high

Page 349

B. It is set to logic low

C. It remains in previous state

D. State of transmission line is not used to start transmission

Question No:175

(Marks:1)

Vu-Topper RM

Demorgan's two theorems prove the equivalency of the NAND and _____ gates and the NOR and _____ gates respectively.

Negative-OR, Negative-AND

Page 74

Question No:176

(Marks:1)

Vu-Topper RM

An Asynchronous Down-counter is implemented (Using J-K flip-flop) by connecting _____.

A. Q output of all flip-flops to J input of next flip-flops

B. Q' output of all flip-flops to K input of next flip-flops

C. Q output of all flip-flops to clock input of next flip-flops

D. Q' output of all flip-flops to clock input of next flip-flops

Question No:177

(Marks:1)

Vu-Topper RM

WHEN BOTH THE INPUTS OF EDGE-TRIGGERED J-K FLOP-FLOP ARE SET TO LOGIC ZERO -----

THE OUTPUT OF FLIP-FLOP REMAINS UNCHANGED

Question No:178

(Marks:1)

Vu-Topper RM

The _____ Encoder is used as a keypad encoder.

Decimal-to-BCD Priority

Page 166

بري صحبت سے تنهائي بهتر ہے اور تنهائي سے نيک صحبت بهتر ہے

For More Help Contact What's app 03224021365

Question No:179 (Marks:1) **Vu-Topper RM**
NOR gate is formed by connecting _____
OR Gate and then NOT Gate **Page 47**

Question No:180 (Marks:1) **Vu-Topper RM**
A particular half adder has
2 INPUTS AND 2 OUTPUT **Page 134**

Question No:181 (Marks:1) **Vu-Topper RM**
Assume a J-K flip-flop has 1s on the J and K inputs. The next clock pulse will cause the output to .
Toggle

Question No:182 (Marks:1) **Vu-Topper RM**
A stage in the shift register consists of
A flip flop

Question No:183 (Marks:1) **Vu-Topper RM**
flip-flops are obsolete now.
Master-Slave

Question No:184 (Marks:1) **Vu-Topper RM**
In Master-Slave flip-flop setup, the master flip-flop operators at
Both Master-Slave operator simultaneously **Page 230**

Question No:185 (Marks:1) **Vu-Topper RM**
The 3-bit up counter can be implemented using _____ flip-flop(s).
A. D-Flip-flop Only
B. S-R Flip-flops Only
C. S-R Flip-flops or D-Flip-flops
D. S-R flip-flops and D-flip-flops **Page 316**

Question No:186 (Marks:1) **Vu-Topper RM**
A transparent mode means _____

بري صحبت سے تڻهائي بهتر هه اور تڻهائي سے نيك صحبت بهتر هه

For More Help Contact What's app 03224021365

- A. Input Hold time is zero (no need to maintain input after clock transition)
- B. The changes in the data at the inputs of the latch are not seen at the output
- C. The changes in the data at the inputs of the latch are seen at the output** **Page 245**
- D. Propagation Delay is zero (Output is immediately changed when clock signal is applied)

Question No:187 (Marks:1) **Vu-Topper RM**
 In _____ outputs depend only on the current state.
Moore Machine **Page 332**

Question No:188 (Marks:1) **Vu-Topper RM**
 Which mechanisms allocate the binary values to the states in order to reduce the cost of the combinational circuits?
State assignment

Question No:189 (Marks:1) **Vu-Topper RM**
 Design of state diagram is one of many steps used to design
A truncated counter

Question No:190 (Marks:1) **Vu-Topper RM**
 The term hold always means.
A. No change
 B. $Q=1, \bar{Q}=0$
 C. $Q=0, \bar{Q}=0$
 D. $Q=0, \bar{Q}=1$

Question No:191 (Marks:1) **Vu-Topper RM**
 A flip-flop is presently in SET state and must remain SET on the next clock pulse. What must j and k be?
 A. $J = 1, K = 0$
B. $J=X(\text{Don'tcare}), K=0$

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

C. $J = 1, K = X$ (Don't care)

D. $J = 0, K = X$ (Don't care)

Question No:192

(Marks:1)

Vu-Topper RM

Invalid state of NOR based SR latch occurs when _____.

S=1, R=1

Question No:193

(Marks:1)

Vu-Topper RM

74HC163 has two enable input pins which are _____ and _____

ENP, ENT

Question No:194

(Marks:1)

Vu-Topper RM

Question No:195

(Marks:1)

Vu-Topper RM

In asynchronous transmission when the transmission line is idle, ____

It is set to logic high

Page 356

Question No:196

(Marks:1)

Vu-Topper RM

LUT is acronym for _____

Look Up Table

Page 439

Question No:197

(Marks:1)

Vu-Topper RM

The three fundamental gates are _____

NOT, OR, AND

Page 40

Question No:198

(Marks:1)

Vu-Topper RM

The total amount of memory that is supported by any digital system depends upon _____

The size of the address bus of the microprocessor

Page 430

Question No:199

(Marks:1)

Vu-Topper RM

In order to synchronize two devices that consume and produce data at different rates, we can use _____

Fist In First Out Memory

Page 425

بري صحبت سے تھائی بہتر ہے اور تھائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:200

(Marks:1)

Vu-Topper RM

A flip-flop changes its state when _____

Low-to-high transition of clock

Page 228

Question No:201

(Marks:1)

Vu-Topper RM

In a sequential circuit the next state is determined by _____ and _____

Input and clock signal applied

Page 305

Question No:202

(Marks:1)

Vu-Topper RM

_____ of a D/A converter is determined by comparing the actual output of a D/A converter with the expected output.

Accuracy

Page 460

Question No:203

(Marks:1)

Vu-Topper RM

Above is the circuit diagram of _____.

Asynchronous up-counter

Page 270

Question No:204

(Marks:1)

Vu-Topper RM

The sequence of states that are implemented by a n-bit Johnson counter is

$2n$ (n multiplied by 2)

Page 354

Question No:205

(Marks:1)

Vu-Topper RM

" $A + B = B + A$ " is _____

Commutative Law

Question No:206

(Marks:1)

Vu-Topper RM

An alternate method of implementing Comparators which allows the Comparators to be easily cascaded without the need for extra logic gates is _____

Using Iterative Circuit based Comparators

Page 155

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Question No:207

(Marks:1)

Vu-Topper RM

DE multiplexer is also called

Data distributor

Page 178

Question No:208

(Marks:1)

Vu-Topper RM

In a state diagram, the transition from a current state to the next state is determined by

Current state and the inputs

Page 332

Question No:209

(Marks:1)

Vu-Topper RM

The alternate solution for a demultiplexer-register combination circuit is

Serial in / Parallel out shift register

Page 356

Question No:210

(Marks:1)

Vu-Topper RM

The storage cell in SRAM is

A capacitor

Page 407

Question No:211

(Marks:1)

Vu-Topper RM

What is the difference between a D latch and a D flip-flop?

The D flip-flop has a clock input.

Question No:212

(Marks:1)

Vu-Topper RM

The _____ of a ROM is the time it takes for the data to appear at the Data Output of the ROM chip after an address is applied at the address input lines

Access Time

Page 417

Question No:213

(Marks:1)

Vu-Topper RM

THE HOURS COUNTER IS IMPLEMENTED USING _____

A SINGLE DECADE COUNTER AND A FLIP-FLOP

Question No:214

(Marks:1)

Vu-Topper RM

The high density FLASH memory cell is implemented using _____

1 floating-gate MOS transistor

Page 419

بري صحبت سے تنهائي بهتر ہے اور تنهائي سے نيک صحبت بهتر ہے

For More Help Contact What's app 03224021365

Question No:215 (Marks:1) **Vu-Topper RM**
Q2 := Q1 OR X OR Q3 The above ABEL expression will be
Q2:= Q1 # X # Q3 **Page 210**

Question No:216 (Marks:1) **Vu-Topper RM**
The output of an AND gate is one when _____
All of the inputs are one **Page 40**

Question No:217 (Marks:1) **Vu-Topper RM**
The binary numbers A = 1100 and B = 1001 are applied to the inputs of a comparator. What are the output levels?
A > B = 1, A < B = 0, A = B = 0 **Page 109**

Question No:218 (Marks:1) **Vu-Topper RM**
The device shown here is most likely a
Multiplexer

Question No:219 (Marks:1) **Vu-Topper RM**
DE multiplexer converts _____ data to _____ data
Serial data, parallel data **Page 356**

Question No:220 (Marks:1) **Vu-Topper RM**
The capability that allows the PLDs to be programmed after they have been installed on a circuit board is called _____
In-System Programming (ISP) **Page 194**

Question No:221 (Marks:1) **Vu-Topper RM**
In _____ outputs depend only on the combination of current state and inputs.
Mealy machine **Page 332**

Question No:222 (Marks:1) **Vu-Topper RM**
In the following statement Z PIN 20 ISTYPE „reg.invert“;

بري صحبت سے تنهائي بهتر ہے اور تنهائي سے نيك صحبت بهتر ہے

For More Help Contact What's app 03224021365

Active-low Registered Mode output

Question No:223

(Marks:1)

Vu-Topper RM

The process of converting the analogue signal into a digital representation (code) is known as _____

Quantization

Page 445

Question No:224

(Marks:1)

Vu-Topper RM

In elevator circuit, the floor display circuit is a combinational circuit which uses the _____ and _____ inputs two determine the floor number and the direction of the display arrow.

- A. OPEN, DIR
- B. MOTION, FB
- C. CONSTATE, FB

D. MOTION and DIR

Page 374

Question No:225

(Marks:1)

Vu-Topper RM

The characteristic equation of D-flip-flop implies that _____.

- A. The next state is independent of inputs
- B. The next state is dependent on present state
- C. The next state is dependent on previous state

D. The next state is independent of the present state.

Page 381

Question No:228

(Marks:1)

Vu-Topper RM

The GAL16V8 has _____.

- A. 16 dedicated inputs
- B. 8 special function pins
- C. 8 pins that are used as inputs or outputs

D. All of the these

Page 200

Question No:229

(Marks:1)

Vu-Topper RM

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

The tri-state buffer connecting the output of the OLMC circuit to the output pin is controlled through _____ different sources.

- A. One
- B. Two
- C. Four**
- D. Three

Page 200

Question No:230

(Marks:1)

Vu-Topper RM

In gated SR latch, what is the value of the output if $EN=1$, $S=0$ and $R=0$?

- A. 1**
- B. 2
- C. 3
- D. 4

Question No:232

(Marks:1)

Vu-Topper RM

To serially shift a byte of data into a shift register, there must be

- A. One load pulse
- B. One clock pulse
- C. Eight clock pulses**
- D. One clock pulse for each 1 in the data

Question No:238

(Marks:1)

Vu-Topper RM

In moore machine the output depends on

- A. Only inputs
- B. The current state**
- C. The current state and inputs
- D. The current state and the output of previous flip flop

Question No:239

(Marks:1)

Vu-Topper RM

A NOR based S-R latches maintain the output state when both the set and reset inputs are _____.

- A. Active
- B. Invalid
- C. Inactive**

Page 215

بري صحبت سے تنہائی بہتر ہے اور تنہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

D. Consistent

Question No:240

(Marks:1)

Vu-Topper RM

The absence of a _____ element in sequential circuit restricts the use of digital combinational circuits to certain application areas.

A. Memory

Page 210

B. Logic

C. Both

D. None

Question No:242

(Marks:1)

Vu-Topper RM

A Quad 1-of-4 MUX has four Multiplexers, each multiplexer has _____ inputs and a single output.

A. 2

B. 4

Page 209

C. 6

D. 8

Question No:243

(Marks:1)

Vu-Topper RM

The _____ description is used to simulate the logic circuit and verify its operation.

A. Logic

B. Test file

C. Test vector

Page 207

D. Declaration

Question No:245

(Marks:1)

Vu-Topper RM

The terminal count of a 4-bit binary counter in the UP mode is _____

A. 1111

B. 0011

C. 0000

D. 1211

بري صحبت سے تہائی بہتر ہے اور تہائی سے نيك صحبت بہتر ہے

For More Help Contact What's app 03224021365

Visit My YouTube Channel
For Subjective and More
Important Notes
Channel Name = #VuTopperRM

برى صحت سے تھائی بہتر ہے اور تھائی سے نیک صحت بہتر ہے

For More Help Contact What's app 03224021365