

CS302-Digital Logic and Design

Solved MCQS for Midterms papers

Solved by JUNAID MALIK and Team



AL-Junaid Institute

Contact no: 03041659294



LMS Handling

Subject Enrollment

- 1) Online classes available
HTML, CSS, Javascript
Python..etc
- 2) Solved Graded Activities
 - Assignment's
 - Quizzes
 - GDB's
- 3) Solved Quiz File's
- 4) Short Note's
- 5) Past paper's &
Current paper's

Website Link

vulmshelp.com

Final project CS619

- 1) SRS
(Software Requirement's
Specification)
- 2) DD
(Design Document)
- 3) Test phase + viva
- 4) Viva preparation
- 5) Final Deliverable

Gmail

junaidfazal08@gmail.com

AL-JUNAID INSTITUTE OF GROUP

1. Which of the following is a volatile memory?

1. PROM
2. DRAM
3. EPROM
4. EEPROM

2. _____ is used when the output is connected back to the input of the PAL or if the output pin is used as an input only.

1. Combinational Input/output
2. Combinational Output
3. Combinational Input
4. Programmable polarity

3. The AND Gate performs a logical _____ function.

1. Addition
2. Subtraction
3. Multiplication
4. Division

4. The Adjacent 1s Detector accepts 4-bit inputs. If _____ adjacent 1s are detected in the input, the output is set to high.

1. 2
2. 4
3. 1
4. 0

5. In the keyboard encoder, how many times per second does the ring counter scan the key board?

1. 600 scans/second
2. 625 scans/second

AL-JUNAID INSTITUTE OF GROUP

3. 650 scans/second

4. 700 scans/second

6. The FAST Model Page Access allows _____ memory read and access times when reading successive data values stored in consecutive locations on the same row.

1. Slow

2. Faster

3. Medium

4. Modern

7. GAL can be reprogrammed as instead of fuses E2CMOS logic is used which can be programmed to connect a _____ with a _____.

1. column, row

2. row, column

3. column, column

4. row, row

8. Which of the following Output Equations determines the output of the State Machine?

1. $MIN = Q0Q1$

2. $MAX = Q0Q1EN$

3. $MIN = Q0Q1EN$

4. $MAX = Q1EN$

9. The maximum value, represented by a single hexadecimal digit is _____.

1. "E"

2. "F"

3. "G"

4. "H"

AL-JUNAID INSTITUTE OF GROUP

10. If the voltage drop across the active load is 0 volts due to absence of current the comparator output is a _____.

1. 0

2. 1

11. The Static Ram (SRAM) is non-volatile and is not a _____ density memory as a latch is required to store a single bit of information.

1. Low

2. High

3. Medium

4. Hot

12. DE Morgan's two theorems prove the equivalency of the NAND and _____ gates and the NOR and _____ gates respectively.

1. Negative-OR, Negative-AND

2. Negative-AND, Positive-OR

3. Positive-OR, Negative-AND

4. Positive-OR, Positive-AND

13. Two signals _____ and _____ provide the timing inputs to the State Machine.

1. NSSR and EWSR

2. LTIME and STIME

3. PTIME and QTIME

4. NSGrn and NSYel

14. The 74HC163 is a 4-bit Synchronous counter, it has _____ data output pins.

1. 2

2. 4

AL-JUNAID INSTITUTE OF GROUP

3. 6

4. 8

- 15. PLDs have In-System Programming (ISP) capability that allows the _____ to be programmed after they have been installed on a circuit board.**

1. PLAs

2. PALs

3. PLDs AL-JUNAID INSTITUTE OF GROUP

4. EPROM

- 16. The CONSTATE.CLK = Clock is used to indicate that the _____ state variables change on a clock transition.**

1. CONSTATE

2. FLOOR

3. MOTION

4. OPEN

- 17. Two types of memories namely the first in-first out (FIFO) memory and last in first out (LIFO) are implemented using _____.**

1. Shift Registers

2. Circular Buffers

3. Ring Buffers

4. Reduce Registers

- 18. The normal data inputs to a flip-flop (D, S and R, J and K, T) are referred to as _____ inputs.**

1. Sequential

2. Asynchronous

3. Synchronous AL-JUNAID INSTITUTE OF GROUP

4. Combinational

AL-JUNAID INSTITUTE OF GROUP

19. For a down counter that counts from (111 to 000), if current state is "101" the next state will be _____.

- 1. 111
- 2. 110
- 3. 010
- 4. None of the given

20. The _____ gate and _____ gate implementation connected at the B input of the 4-bit Adder is used to allow Complemented or Un-Complemented B input to be connected to the Adder input.

- 1. AND, NOR
- 2. AND, NOT
- 3. AND, OR
- 4. XOR, NAND

21. The Synchronous SRAM also has a Burst feature which allows the Synchronous SRAM to read or write up to _____ location(s) using a single address.

- 1. One
- 2. Two
- 3. Three
- 4. Four

22. In NAND based S-R latch, output of each _____ gate is connected to the input of the other _____ gate.

- 1. NOR, NAND
- 2. NAND, NOR
- 3. NOR, NOR
- 4. NAND, NAND

AL-JUNAID INSTITUTE OF GROUP

23. Implementing the Adjacent 1s detector circuit directly from the function table based on the SOP form requires _____ gates for the 8 product terms (minterms) with an 8-input OR gate.

1. 8 OR
2. 8 AND
3. 8 XOR
4. 8 NOR

24. 8-bit parallel data can be converted into serial data by using _____ multiplexer.

1. 4-to-2
2. 8-to-1
3. 4-to-4
4. 8-to-4

25. The _____ input overrides the _____ input.

1. Asynchronous, synchronous
2. Synchronous, asynchronous
3. Preset input (PRE), Clear input (CLR)
4. Clear input (CLR), Preset input (PRE)

26. A SOP expression can be implemented by an _____ combination of gates.

1. OR-XOR
2. AND-NAND
3. AND-OR
4. XOR-NOR

27. The 64-cell array organized as 8 x 8 cell array is considered

1. as an 64 byte memory
2. as a 16 byte memory

AL-JUNAID INSTITUTE OF GROUP

3. as an 8 byte memory
4. as an 4 byte memory
28. The terminal count of a 4-bit binary counter in the UP mode is _____.
1. 1100
2. 0011
3. 1111
4. 0000
29. A 3-variable karnaugh map has
1. eight cells
2. three cells
3. sixteen cells
4. four cells
30. An Asynchronous Down-counter is implemented (Using J-K flip-flop) by connecting _____.
1. Q output of all flip-flops to clock input of next flip-flops
2. Q' output of all flip-flops to clock input of next flip-flops
3. Q output of all flip-flops to J input of next flip-flops
4. Q' output of all flip-flops to K input of next flip-flops
31. Memory is arranged in _____.
1. linear fashion
2. two-dimensional manner
3. three-dimensional manner
4. random fashion
32. If two numbers in BCD representation generate an invalid BCD number then the binary _____ is added to the result.
1. 1001
2. 0110

AL-JUNAID INSTITUTE OF GROUP

AL-JUNAID INSTITUTE OF GROUP

3. 1111

4. 1100

33. Subtractors also have output to check if 1 has been _____.

1. Primed

2. Shifted

3. Complemented

4. Borrowed

34. The Test Vector definition defines the test vectors for all the three counter inputs and _____ counter output/outputs.

1. One

2. Two

3. Three

4. Four

35. A multiplexer with a register circuit converts

1. Serial data to parallel

2. Parallel data to serial

3. Serial data to serial

4. Parallel data to parallel

36. A decade counter can be implemented by truncating the counting sequence of a MOD-20 counter.

1. True

2. False

37. The n flip-flops store _____ states.

1. 1

2. 2^n

3. 0

4. $2^{(n+1)}$

AL-JUNAID INSTITUTE OF GROUP

38. The S-R latch has two inputs, therefore _____ different combinations of inputs can be applied to control the operation of the S-R latch.

1. two
2. four
3. eight
4. sixteen

39. Why demultiplexer is called a data distributor?

1. The input will be distributed to one of the outputs
2. The input will be selected for the output
3. The output will be distributed to one of the inputs
4. Single input to Single Output

40. When the transmission line is idle in an asynchronous transmission

1. It is set to logic low
2. It is set to logic high
3. It remains in previous state
4. State of transmission line is not used to start transmission

41. UVERPROM is stands for

1. Ultra-Variant
2. Ultra-Vibrant
3. Ultra-Voilet
4. Ultra-Visible

42. In memory write cycle, the time for which the WE signal remains active is known as the _____.

1. Write address setup
 2. Write pulse width
- AL-JUNAID INSTITUTE OF GROUP

AL-JUNAID INSTITUTE OF GROUP

3. Write delay width

4. Write data time

43. The outputs of SR latches in elevator state machine are feed back to the _____ gate array for connection to the D-flipflops.

1. NOT

2. AND

3. OR

4. XOR

44. PALs tend to execute _____ logic.

1. SPD

2. SOP

3. SAC

4. SAP

45. The ROM used by a computer is relatively _____ as it stores few byres of code used to Boot the Computer system on power up.

1. Small

2. Large

3. Heavy

4. High

46. Which signal must remain valid in memory write cycle after data is applied at the data input lines and must remain valid for a minimum time duration tWD?

1. $\overline{\text{CS}}$

2. $\overline{\text{WE}}$

3. W

4. OE

47. You have to choose suitable option when your timer will reset by considering this given code:

AL-JUNAID INSTITUTE OF GROUP

TRSTATE.CLK = clk;

TMRST: = (TRSTATE == NSY2) # (TRSTATE == EWY2);

1. NSY2 or EWY2
2. NSSR or TMRST
3. EWSR or NSRED
4. EWRed or EWYel

48. A NOR based S-R latch is implemented using _____ gates instead of _____ gates.

1. XOR, NAND
2. NOR, XOR
3. NOR, NAND
4. OR, XOR

49. Implementation of Latch is required almost _____ transistor.

1. Two
2. Four
3. Six
4. Eight

50. In distributed mode, for a 1024 x 1024 DRAM memory and a refresh cycle of 8 msec, each of the 1024 rows has to be refreshed in _____ when Distributed refresh is used.

1. 4.8 microsec
2. 5.9 microsec
3. 7.8 microsec
4. 5.5 microsec

51. The NOR logic gate is the same as the operation of the _____ gate with an inverter connected to the output.

AL-JUNAID INSTITUTE OF GROUP

1. AND
2. NAND
3. OR
4. NOT

52. For a Standard SOP expression, a _____ is placed in the cell corresponding to the product term (Minterm) present in the expression.

1. 0
2. 1
3. x (don't care condition)
4. Any of given option depending on SOP term

53. Select the mode of programming in which GAL16V8 can be programmed:

1. Simple Mode
2. Complex Mode
3. Registered Mode
4. All of the given

54. Divide-by-32 counter can be achieved by using

1. Flip-Flop and DIV 10
2. Flip-Flop and DIV 16
3. Flip-Flop and DIV 32
4. DIV 16 and DIV 32

55. The next state table for REQ1, FLOOR1 and OPEN inputs indicates that the _____ can be pressed at any time either on the first floor or the second floor in elevator.

1. REQ0
2. OPEN
3. REQ1
4. FLOOR1

AL-JUNAID INSTITUTE OF GROUP

AL-JUNAID INSTITUTE OF GROUP

56. Consider $A=1$, $B=0$, $C=1$. A, B and C represent the input of three bit NAND gate, the output of the NAND gate will be _____.

1. Zero
2. One
3. Undefined
4. No output as input is invalid

57. A 4-bit binary up/down counter is in the binary state of zero. The next state in the DOWN mode is:

1. 0001
2. 1000
3. 1110
4. 1111

58. Adding two octal numbers "36" and "71" result in _____.

1. 213
2. 123
3. 127
4. 345

59. The ABEL Input file can use a _____ instead of the equation to specify the Boolean expressions.

1. Truth Table
2. State Diagram
3. Karnaugh Map
4. Logic Circuit

60. The domain of the expression $AB'CD + AB' + C'D + B$ is

1. A and D
2. B only

AL-JUNAID INSTITUTE OF GROUP

3. A, B, C and D

4. None of the given

61. If the number of samples that are collected is reduced by half, the reconstructed signal will be _____ from/to the original.

1. Different

2. Same

3. Equal

4. Opposite

62. In DRAM read cycle R /W- signal is activated to read data which is made available on the _____ data line.

1. D(IN)

2. D(OUT)

3. D(AB)

4. D(INT)

63. In case of cascading Integrated Circuit counters, the enable inputs and RCO of the Integrated Circuit counters allow cascading of multiple counters together.

1. True

2. False

64. Implementation of the FIFO buffer in _____ is usually takes the form of a circular buffer.

1. RAM AL-JUNAID INSTITUTE OF GROUP

2. ROM

3. PPR0M

4. Flash Memory

65. As data values are written or read from the RAM Stack Pointer Register increments or decrements its contents always pointing to the stack _____.

AL-JUNAID INSTITUTE OF GROUP

1. Bottom

2. Top

3. Down

4. Vertex

66. Which one flip-flop has an invalid output state?

1. T

2. JK

3. SR

4. D

67. The output of a NAND gate is _____ when all the inputs are one.

1. Zero

2. One

3. Available

4. Not available

68. The Transition table is very similar to the _____ table.

1. Truth

2. State

3. Transition

4. None of the given

69. Consider the sum of weight method for converting decimal into binary value, _____ is the highest weight for 411.

1. 64

2. 128

3. 256

4. 512

70. Canonical form is a unique way of representing _____.

AL-JUNAID INSTITUTE OF GROUP

1. SOP

2. Minterm

3. Boolean Expression

4. POS

71. _____ Counters as the name indicates are not triggered simultaneously.

1. Asynchronous

2. Synchronous

3. Positive-Edge triggered

4. Negative-Edge triggered

72. Cin is part of _____ Adder.

1. Half

2. Full

3. Single

4. Double

73. Flash memory Operation are classified into _____ different operation.

1. Two

2. Three

3. Four

4. Five

1. A Product term is 0 when _____

a. Any one literal is 0

b. Any of the literals is 1

c. At least two literals are 1

d. All the literals are 1

2. In 8-input multiplexer, the two outputs are connected through a/an _____ gate.

AL-JUNAID INSTITUTE OF GROUP

a. AND

5. OR AL-JUNAID INSTITUTE OF GROUP

b. NOT

c. NOR

3. ____ Device dissipate varying amount of power depending upon the frequency of operation.

a. TTL

b. CMOS

c. Storage

d. Peripheral

4. Boolean Addition operation is performed by a(an) ____ gate.

a. AND

b. OR

c. XOR

d. NAND

5. A SOP expression can be implemented by an ____ combination of gates.

a. OR-XOR

b. AND-AND

c. AND-OR

d. XOR-NOR

6. The maximum decimal number that can be represented using the 64-bit unsigned representation is ____.

a. 2^{63}

AL-JUNAID INSTITUTE OF GROUP

b. $(2^{64})-1$

c. $(2^{64}+$

d. 2^{64}

7. In 16-bit ALU, The G output is activated if the 4-bit unit generate a Carry ____ irrespective of Carry ____.

a. In, In

b. In, Out

c. Out, In

d. Out, Out

8. A standard POS form has ____ terms that have all the variables in the domain of the expression.

a. Sum

b. Product

c. Min

d. Composite

9. In Cascading Priority Encoders, the EO output is connected to the EI input of the encoder which handles ____.

a. Lower priority outputs

b. Higher priority outputs

c. Lower priority inputs

d. Higher priority inputs

10. Which of the following is the example of comparator?

a. OR

b. AND

c. XOR

AL-JUNAID INSTITUTE OF GROUP

d. XNOR

11. IN CMOS 5 Volt series, Input voltage of Logic high signal (VIH) with a ranges from ____ to ____ volts.

- a. 4,5,5
- b. 0 ,5
- c. 0,3,5

d. 3,5,5

12. The Adjacent 1 S Detector accepts 4-bits input. If ____ adjacent 1S are detected in the input, the output is set to high.

- a. 2

b. 4

- c. 1
- d. 0

13. DE Morgan's two theorems prove the equivalency of the NAND and ____ gates and the NOR and ____ gates respectively.

- a. Negative-OR, Negative-AND

b. Negative-AND, Negative-OR

- c. positive-OR, Negative-AND
- d. positive-AND, Negative-OR

14. Adding two octal numbers "36 and 71" result in ____.

- a. 213
- b. 123

c. 127

- d. 345

AL-JUNAID INSTITUTE OF GROUP

15. Any of the _____ forms of the Karnaugh Map can be used to simplify Boolean expressions

a. Three

b. Four

c. Two

d. Five

16. Quine-McCluskey and K-Map methods are used for _____ of Boolean expression.

a. Multiplication

b. Addition

6. Simplification

AL-JUNAID INSTITUTE OF GROUP

c. Subtraction

17. The number "1259" may belong to _____ number system.

a. Binary number system

b. Octal or Decimal system

c. Decimal or Hexadecimal system

d. Binary or Hexadecimal system

18. The series of TTL chips are characterized by their _____.

a. Switching Speed only

b. Power Dissipation only

c. Both

d. None of these

19. All ABEL statements must end with _____.

AL-JUNAID INSTITUTE OF GROUP

a. :

b. ,

c. ;

d. “

20. In sequential circuit memory elements are connected with ____.

a. Logical circuit

b. Clock

c. Feedback path

d. External Event

21. In the 32-bit Single Precision Floating Point format, the exponent value ____ is reserved to represent infinity exponents.

a. 98

b. 99

c. 255

d. 256

22. The ____ output has the output of the OR gate connected through an XOR gate to the tri-state buffer.

a. Combinational

b. Combinational input/

c. PLA

d. None

23. The limitation in implementation of parallel binary address is known as ____.

a. Delay

b. Carry propagation

c. Carry input

AL-JUNAID INSTITUTE OF GROUP

d. Carry output

24. The Gray code is different from the unsigned binary code

because_____.

a. Successive value of Gray code by only one bit

b. Gray code is positional code

c. Gray code not support negative values

d. Gray code ranges from "0" to "9"

25. Removing the NOT gate at the output of the NOR gate result in an_____.

7. OR gate

AL-JUNAID INSTITUTE OF GROUP

a. NAND gate

b. AND gate

c. NOT gate

26. Portable devices that run on batteries use_____ circuit that have low power dissipation.

a. Series

b. Integrated

c. Parallel

d. Electric

27. The domain of the expression $AB'CD+B$ is

a. A and D

b. A,B,C and D

c. C and D only

AL-JUNAID INSTITUTE OF GROUP

d. B only

28. _____ is a single input gate

a. AND

b. OR

c. NOT

d. XOR

29. To represent in digital value, the number of digit (0s and 1s) that represent a quantity is _____ to the range of values that are to be represented.

a. Equal

b. Greater

c. Lesser

d. Not equal

30. BCD code of 16 is _____.

a. 10001

b. 00010001

c. 00010111

d. 01110001

31. To determine the seven expressions for each of the seven outputs in 7-segment display, seven _____ variable Karnaugh Maps are used.

8. 3

AL-JUNAID INSTITUTE OF GROUP

a. 4

AL-JUNAID INSTITUTE OF GROUP

b. 5

c. 2

32. In Odd parity generator circuit which gate is used to detect parity errors?

a. OR

b. NOR

c. XOR

d. AND

33. A 3-variable Karnaugh map has

a. Eight cells

b. Three cells

c. Sixteen cells

d. Four cells

34. The measurable values generally change over a

a. Specified period

b. Discrete range

c. Time

d. Continuous range

35. _____ uses E2CMOS technology which is Electrically Erasable CMOS

instead of Bipolar technology and fusible links.

a. PAL

b. GAL

AL-JUNAID INSTITUTE OF GROUP

- c. PLA
 - d. PROM
36. When the number 29 is represent on 7-segment display, which BCD input is represented on LSD display unit?
- a. 1000
 - b. 1001**
 - c. 1010
 - d. 1100
37. How many of enable inputs is(are) active-low in 74xx138 3 to 8 Decoder?
- a. One
 - b. Two
 - c. Three**
 - d. Four
38. The simplified expression using either of the two K-maps are_____.
- a. Similar
 - b. Different
 - c. Identical**
 - d. None-identical
39. Which of the following expression in the product of sums form?
- a. $(A + B)(C + D)$
 - b. $(AB)(CD)$

AL-JUNAID INSTITUTE OF GROUP

AL-JUNAID INSTITUTE OF GROUP

c. $AB(CD)$

d. $AB+CD$

40. CMOS technology is characterized by low power dissipation with _____ switching speeds.

a. Slow

b. Fast

c. Average

d. Medium

41. Two 2-bit comparator circuits can be connected to form single 4-bit comparator

a. True

b. False

42. High level Noise Margins (VNH) of CMOS 5 volt series circuits is _____

a. 0.2 V

b. 0.5 V

c. 0.9 V

d. 3.3 V

43. The output of the expression $F=A+B+C$ will be Logic _____

when $A=0$, $B=1$, $C=1$. the symbol "+" here represents OR Gate

AL-JUNAID INSTITUTE OF GROUP

a. Undefined

b. One

c. Zero

d. 10(binary)

44. If an active-HIGH S-R latch has a 0 on the S input and a 1 on the R input and then the R input goes to 0, the latch will be _____.

a. SET

b. RESET

c. Clear

d. Invalid

45. 3.3 v CMOS series is characterized by _____ and _____ as compared to the 5 v CMOS series.

a. Low switching speeds, high power dissipation

b. Fast switching speeds, high power dissipation

c. Fast switching speeds, very low power dissipation (page61)

d. Low switching speeds, very low power dissipation

46. The binary value "1010110" is equivalent to decimal _____

a. 86

b. 87

c. 88

d. 89

47. The _____ Encoder is used as a keypad encoder.

AL-JUNAID INSTITUTE OF GROUP

- a. 2-to-8 encoder
- b. 4-to-16 encoder
- c. BCD-to-Decimal

d. Decimal-to-BCD Priority

48. How many data select lines are required for selecting eight inputs?

- a. 1
- b. 2
- c. 3**
- d. 4

49. The Quad Multiplexer has _____ outputs

- a. 4**
- b. 8
- c. 12
- d. 16

50. Demultiplexer has

- a. Single input and single outputs.
- b. Multiple inputs and multiple outputs.

c. Single input and multiple outputs.

- d. Multiple inputs and single output.

51. The expression _____ is an example of Commutative Law for Multiplication.

- a. $AB+C = A+BC$
- b. $A(B+C) = B(A+C)$

AL-JUNAID INSTITUTE OF GROUP

c. $AB=BA$

d. $A+B=B+A$

52. The look-ahead carry circuits_____

a. Add a 1 to complemented inputs

b. Reduce propagation delay

c. Increase ripple delay

d. Determine sign and magnitude

53. What is the output expression of segment 'b' implementation in BCD to 7-segment decoder?

a. $B+C'D'+CD$

b. $B'+C'D'+CD$

c. $B+C'D'+C'D$

d. $B'+C'D'+CD'$

54. 2-input, 8-bit Multiplexer, by setting the S input to logic_____

the_____ inputs of both the multiplexers are selected.

a. Low

b. High, B

c. Low, C

d. Low, C

55. The maximum decimal number that can be represented using the

64-bit unsigned representation_____

AL-JUNAID INSTITUTE OF GROUP

- a. 2^{63}
 - b. $(2^{64})-1$
 - c. $(2^{64})+1$
 - d. 2^{64}
56. When two or more products terms are assumed by Boolean addition, the result is a ____
- a. POS
 - b. SOP
 - c. Boolean
 - d. Simplified
57. Tri-State Buffer is a ____ gate with a control line that disconnects the
- a. OR
 - b. AND
 - c. NAND
 - d. NOT
58. The 4-bits 2's complement representation of "7" is _____
- a. 0111
 - b. 1111
 - c. 1001
 - d. 0110
59. _____ and _____ are the steps of the Quine-McCluskey.

AL-JUNAID INSTITUTE OF GROUP

- a. Draw a table and make groups
 - b. Write binary codes and write SOP
 - c. Find prime implicants and select minimal set of the prime implicants.
 - d. None of the given
60. The binary number 1011,101 has an Integer part represented by _____ and a fraction part ____ separated by a decimal point.
- a. 1011,101
 - b. 101,1011
 - c. 101,1101
 - d. 10111,11
61. Subtractors also have output to check if 1 has been _____
- a. Primed
 - b. Shifted
 - c. Complemented
 - d. Borrowed
62. CMOS technology is characterized by low power dissipation with _____ switching speeds.
- a. Slow
 - b. Fast
 - c. Average
 - d. Medium
63. The _____ description is used to simulate the logic circuit and verify its operation.

AL-JUNAID INSTITUTE OF GROUP

- a. Test file
- b. Declaration
- c. Logic
- d. Test vector

64. How many outputs can an integrated circuit comparator have?

- a. One
- b. Two
- c. Three
- d. Four

65. Which of the following is not the correct method of grouping?

- a. Along adjacent columns
- b. On comers
- c. Diagonally
- d. Along adjacent rows

66. The output of the expression $F=A.B.C$ will be logic _____
when $A=1, B=0, C=1$.

- a. Undefined
- b. One
- c. Zero
- d. No output as input is valid

AL-JUNAID INSTITUTE OF GROUP

67. The _____ gate and _____ gate implementation connected at the B

input of the 4-bit Adder is used to allow complemented or Un-Complemented B input to be connected to the Adder input.

- a. AND,NOR
- b. AND,NOT
- c. AND,OR
- d. XOR,NAND

68. In the 32-bit Single Precision Floating point format, the exponent value _____ is reserved infinity exponent.

- a. 98
- b. 99
- c. 255
- d. 256

69. The Boolean expression $(AB'CS')$ is used

- a. A sum term
- b. A product term
- c. A literal term
- d. A max term

70. The product of an XOR gate is zero(0), when _____

- I. All the inputs are zero
- II. Any of the inputs is zero

AL-JUNAID INSTITUTE OF GROUP

III. An of the inputs is one IV.

All the inputs are one

- a. I only
- b. IV only
- c. I and IV only
- d. II and III

71. _____ methods are used to Convert Decimal fractions to Binary.

- a. 1
- b. 2
- c. 3
- d. 4

72. To display the number _____ the BCD number 0010 representing the MSD is applied at the inputs of the BCD to 7-segment display circuit connected to the MSD &-Segment Display digit

- a. 19
- b. 29
- c. 39
- d. 49

73. The look-ahead carry circuits _____

- a. Add a 1 to complemented inputs
- b. Reduce propagation delay
- c. Increase ripple delay

AL-JUNAID INSTITUTE OF GROUP

- d. Determine sign and magnitude.
- 74.** If two numbers in BCD representation generate an invalid BCD number then the binary ___ is added to the result
- a. 1001
 - b. 0110**
 - c. 1111
 - d. 1100
- 75.** Both the multiplexers are selected simultaneously when _____ is set to logic _____ in 2-inputs, 8-bit Multiplexer.
- a. G, Low
 - b. G, High
 - c. S, Slow
 - d. S, High
- 76.** Function labels required to represent the input/output combinations for each segment in 7-segment display
- a. 5
 - b. 7**
 - c. 8
 - d. 10
- 77.** Multiplexers are also known as _____
- a. Data distributors
 - b. Data selectors**
 - c. Data manipulators

AL-JUNAID INSTITUTE OF GROUP

d. Data setters

78. The PLA can be programmed to give an output of constant

_____ or _____

a. 0,1

b. 1,2

c. 2,3

d. 0,0

79. Cin is part of _____ Adder.

a. Half

b. Full

c. Single

d. Double

80. The look-ahead carry circuits _____

a. Add 1 to complemented inputs

b. Reduce propagation delay

c. Increase ripple delay

d. Determine sign and magnitude

81. Which of the following gates has the outputs 1 if and only if at least one input is 1?

a. AND

AL-JUNAID INSTITUTE OF GROUP

- b. NOR
- c. NAND
- d. OR

82. A sop expression can be implemented by on ____ combination of gates.

- a. OR-XOR
- b. AND-NAND
- c. AND-OR
- d. XOR-NOR

83. The carry, instead of rippling through the 4-bits of the individual ALU circuit, has to propagate through ____ ALU units in 16-bit ALU.

- a. Two
- b. Four
- d. 9

91. Digital circuits operates with _____ voltage value(s)

- a. 1
- b. 2
- c. 3
- d. 4

92. Which of the following is the octal equivalent of 28 decimal numbers?

- a. 31
- b. 32

AL-JUNAID INSTITUTE OF GROUP

c. 33

d. 34

93. In cascading Priority Encoders, the EO output is connected to the EI of the encoder which handles _____

a. Lower priority outputs

b. Higher priority outputs

c. Lower priority inputs

d. Higher priority inputs

94. To determine the seven expressions for each of the seven outputs in

7-segment display, seven _____ variable Karnaugh maps are used.

a. 3

b. 4

c. 5

d. 2

95. The output of a NAND Gate is _____ when all the inputs are one.

a. Zero

b. One

c. Available

d. Not available

96. The _____ is the slowest and consumes more power.

a. Standard TTL

AL-JUNAID INSTITUTE OF GROUP

- b. Schottky TTL
 - c. Advanced Schokottky TTL
 - d. Low-Power Schottky TTL
97. The between expression $X-AB+CD$ represents
- a. Two Ors ANDed together
 - b. A 4-input AND gate
 - c. Two ANDs ORed together
 - d. An eclusive-OR
98. The expression $F-A+B+C$ describes the operation of three bits ____ Gate.
- a. OR
 - b. AND
 - c. NOT
 - d. NAND
99. Which one of the following is NOT a valid rule of Boolean Algebra?
- a. $A+1=1$
 - b. $A=A'$
 - c. $AA=A$
 - d. $A+0=A$
100. A 5-Variable Karnaugh map has
- a. Sixteen cells
 - b. Thirty two cells
 - c. Sixty four cells
 - d. None of these

AL-JUNAID INSTITUTE OF GROUP

101. _____ is invalid number of cells in a single group formed by the adjacent cells K-map
- a. 2
 - b. 8
 - c. 12
 - d. 16
102. In 32-bit Single –Precision floating point format representation the range of exponent value is from _____ to _____
- a. +127 to -126
 - b. +127 to -254
 - c. +128 to -254
 - d. +256 to -255
103. _____ has the fastest switching speed and low power requirements
- a. Advanced low power schottky
 - b. Fast TTL
 - c. Standard TTL
 - d. Schottky TTL