

VIRTUAL UNIVERSITY OF PAKISTAN

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922
TEAM HADI(VU LAHORE)

MID TERM PAST PAPER

We Deal All Kind of VU Project
(PHP, .NET, ANDROID, PYTHON)

MADE AND SOLVED BY HADI

WARNING: Team HADI is not responsible for any mistake or wrong answer. All students reading and using this document may check and confirm the answers at their own.



WhatsApp: 03087122922



FACEBOOK ID: <https://www.facebook.com/hadipastpapers/>

Best of luck!



Question No : 1 of 26

Marks: 1 (Budgeted Time 1 Min)

The range of Excess-8 code is from _____ to _____.

Answer (Please select your correct option)

☐ +7 to -8

correct

☐ +8 to -7

☐ +9 to -8

☐ -9 to +8

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 2 of 26

Marks: 1 (Budgeted Time 1 Min)

The decimal "17" in BCD will be represented as _____

Answer (Please select your correct option)

☐ 11101

☐ 11011

☐ 10111

correct

☐ 11110

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 3 of 26

Marks: 1 (Budgeted Time 1 Min)

The four outputs of two 4-input multiplexers, connected to form a 16-input multiplexer, are connected together through a 4-input _____ gate

Answer (Please select your correct option)

☐ AND

☐ OR

correct

☐ NAND

☐ XOR

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 4 of 26

Marks: 1 (Budgeted Time 1 Min)

A standard interface for programming the In-System PLD consists of _____.

Answer (Please select your correct option)

☐ 2-wire

☐ 4-wire

correct

☐ 8-wire

☐ 16-wire

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 5 of 26

Marks: 1 (Budgeted Time 1 Min)

_____ Dual, 4-input multiplexer can be connected to form a 16-input multiplexer.

Answer (Please select your correct option)

☐ 2

☐ 3

☐ 4

correct

☐ 5

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 6 of 26

Marks: 1 (Budgeted Time 1 Min)

S-R latch can be implemented by using _____ gates

Answer (Please select your correct option)

☐ AND, OR

correct

☐ NAND, NOR

☐ NAND, XOR

☐ NOT, XOR

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 7 of 26

Marks: 1 (Budgeted Time 1 Min)

A product term is 0 when _____.

Answer (Please select your correct option)

☐ Any of the literals is 1

☐ At least two literals are 1

☐ All the literals are 1

☐ Any of the literal is 0

correct

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 8 of 26

Marks: 1 (Budgeted Time 1 Min)

What will be the output of a 3-input NAND gate for the input values: A=1, B=0, C=1

Answer (Please select your correct option)

- ☐ Zero
- ☐ One
- ☐ Undefined
- ☐ No output, as input is invalid

correct

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 9 of 26

Marks: 1 (Budgeted Time 1 Min)



_____ is not a valid hexadecimal number.

Answer (Please select your correct option)

☐ 1234

☐ ABCD

☐ 1001

☐ DEHF

correct

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 10 of 26

Marks: 1 (Budgeted Time 1 Min)

2's complement of any binary number can be calculated by

Answer (Please select your correct option)

- ☐ adding 1 to 1's complement
- ☐ subtracting 1 from 1's complement.
- ☐ calculating 1's complement and inverting Most significant bit
- ☐ adding 1's complement twice

correct

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL-hadirajputofficial@gmail.com
WHATSAPP& CALL-03087122922

MADE BY HADI

Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 11 of 26

Marks: 1 (Budgeted Time 1 Min)

A BCD to 7-Segment decoder has _____ inputs and _____ outputs.

Answer (Please select your correct option)

☐ 3, 7

☐ 4, 7

correct

☐ 7, 3

☐ 7, 4

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 12 of 26

Marks: 1 (Budgeted Time 1 Min)

Which of the following simplification method is intended to be used for Boolean expressions having more than four variables?

Answer (Please select your correct option)

☐ Boolean Algebra and rules

☐ Karnaugh Map

☐ Quine-McCluskey

correct

☐ Demorgan's Theorem


MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

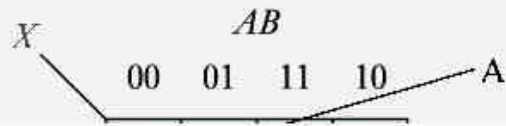Question No : 13 of 26

Marks: 1 (Budgeted Time 1 Min)

In the following Karnaugh map, which group has "legal grouping" ?



Answer (Please select your correct option)

☐ A

☐ B

☐ C

correct

☐ D

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 13 of 26

Marks: 1 (Budgeted Time 1 Min)

	00	1	1	1	0	
	01	1	0	0	1	
CD	11	0	1	1	1	

Diagram showing a 3x5 grid with values. The grid is labeled with 'CD' on the left. The values are: Row 00: [1, 1, 1, 0]; Row 01: [1, 0, 0, 1]; Row 11: [0, 1, 1, 1]. Four regions are highlighted with blue boxes and labeled A, B, C, and D: A is the first column (1, 1, 0); B is the top-right corner (1, 1); C is the middle-right corner (0, 0, 1); D is the bottom-right corner (1, 1, 1).

Answer (Please select your correct option)

A

☐

B

☐

C

☐

D

☐

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 13 of 26

Marks: 1 (Budgeted Time 1 Min)

11	0	1	1	1
10	0	1	1	0

D

Answer (Please select your correct option)

A

☐

B

☐

C

☐

D

☐

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

What are the values of sum and carry out when two 4-bit binary numbers (1011 and 1111) are applied to a 4-bit parallel adder and carry input is 1.

Answer (Please select your correct option)

☐ $\Sigma_4 \Sigma_3 \Sigma_2 \Sigma_1 = 0111, C_{out} = 0$

☐ $\Sigma_4 \Sigma_3 \Sigma_2 \Sigma_1 = 1111, C_{out} = 1$

☐ $\Sigma_4 \Sigma_3 \Sigma_2 \Sigma_1 = 1011, C_{out} = 1$

☐ $\Sigma_4 \Sigma_3 \Sigma_2 \Sigma_1 = 1100, C_{out} = 1$

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 15 of 26

Marks: 1 (Budgeted Time 1 Min)

A particular half-adder has _____ inputs and _____ output(s).

Answer (Please select your correct option)

☐ 3, 1

☐ 3, 2

☐ 2, 1

☒ 2, 2

correct

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 16 of 26


Marks: 1 (Budgeted Time 1 Min)

TTL based devices work with a DC supply of ____ Volts

Answer (Please select your correct option)

☐ +10

☒ +5

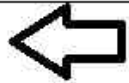

correct

☐ +3

☐ 3.3

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 17 of 26


Marks: 1 (Budgeted Time 1 Min)

In CMOS 5 Volt series, Input voltage for Logic high signal (V_{IH}) is in the range of _____ volts.

Answer (Please select your correct option)

☐ 3.5 to 5

correct

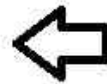

☐ 4.5 to 5

☐ 0 to 5

☐ 0 to 3.5

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP & CALL: 03087122922

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 18 of 26

Marks: 1 (Budgeted Time 1 Min)

A multiplexer circuit has _____ input(s) and _____ output(s).

Answer (Please select your correct option)

☐ Single, single

☐ Single, multiple

☐ Multiple, single

☒ Multiple, multiple



correct

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 19 of 26

Marks: 1 (Budgeted Time 1 Min)


The binary values for the standard SOP expression, $AB\bar{C}\bar{D} + \bar{A}BC\bar{D} + \bar{A}\bar{B}\bar{C}D$ are _____

Answer (Please select your correct option)

☐

1110 + 0110 + 0001

correct

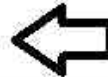

☐

1011 + 1111 + 1011

☐

0001 + 1001 + 1110

☐

1010 + 1110 + 0101

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122922 (Team Hadi Lahore)

Question No : 20 of 26

Marks: 1 (Budgeted Time 1 Min)

Determine the binary values of the variables for the following standard POS expression.
 $(A + \bar{B} + C)(\bar{A} + B + \bar{C})$

Answer (Please select your correct option)

☐ $(1 + 0 + 1)(0 + 1 + 0)$

correct



☐ $(0 + 1 + 0)(1 + 0 + 1)$

☐ $(1 + 0 + 0)(0 + 0 + 1)$

☐ $(0 + 1 + 0)(1 + 1 + 0)$

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 21 of 26

Marks: 2 (Budgeted Time 4 Min)

How many possible outputs does a decoder of 3 inputs contain?

Answer ([Please click here to Add Answer](#))



MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 22 of 26

Marks: 2 (Budgeted Time 4 Min)

How can we use 3-to-8 decoder to implement SOP expressions?

Answer ([Please click here to Add Answer](#))



MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 23 of 26

Marks: 3 (Budgeted Time 6 Min)

For a two bit comparator circuit, specify all the inputs for which $A > B$ is set to 1.

Answer ([Please click here to Add Answer](#))




MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

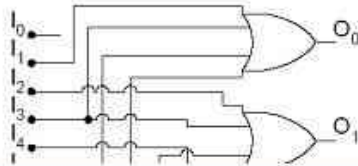Question No : 24 of 26

Marks: 3 (Budgeted Time 6 Min)

Identify the following circuit that is which combinational circuit is being represented by this diagram?



Answer ([Please click here to Add Answer](#))




MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 24 of 26

Marks: 3 (Budgeted Time 6 Min)

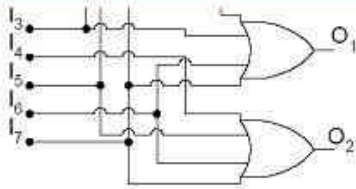

Answer ([Please click here to Add Answer](#))



MADE BY HADI

Email: hadirainutoofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 25 of 26

Marks: 5 (Budgeted Time 10 Min)

Consider a logical circuit for 4-bit binary number. The circuit gives output 0 for adjacent 0s in a binary number. Draw the karnaugh map of such circuit and derive simplified POS expression.

Answer ([Please click here to Add Answer](#))



MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 26 of 26

Marks: 5 (Budgeted Time 10 Min)

Multiplexers can be used as a "Logic Function Generator". Draw only circuit diagram and function table based on three variables.

Answer ([Please click here to Add Answer](#))



MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

HADI VU PAST PAPER

WE DEAL ALL KIND OF VU PROJECT
(PHP, ANDROID, PYTHON)

DEAR STUDENTS

ARE YOU LOOKING
FOR ASSISTANCE

- 1) ASSIGNMENTS
- 2) QUIZZES
- 3) GDB
- 4) GRAND QUIZZES

We Provide, You Solution
of VU Academic Activities
include Assignments,
Quizzes, GDBs, Grand Quizzes
If You Need Help in Services
Kindly inform us.

TEAM HADI
(VU LAHORE)



TEAM HADI
(VU LAHORE)



HADI TECH

#PAID_TASK

CONTACT US

CALL & WHATSAPP

0308-7122922