

VIRTUAL UNIVERSITY OF PAKISTAN

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922
TEAM HADI(VU LAHORE)

MID TERM PAST PAPER

We Deal All Kind of VU Project
(PHP, .NET, ANDROID, PYTHON)

MADE AND SOLVED BY HADI

WARNING: Team HADI is not responsible for any mistake or wrong answer. All students reading and using this document may check and confirm the answers at their own.



WhatsApp: 03087122922



FACEBOOK ID: <https://www.facebook.com/hadipastpapers/>

Best of luck!



Question No : 1 of 26

Marks: 1 (Budgeted Time 1 Min)

Consider the binary number "100101", its 2's complement will be _____.

Answer (Please select your correct option)

☐ 100110

☐ 011011

correct

☐ 100111

☐ 011010

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 2 of 26

Marks: 1 (Budgeted Time 1 Min)

The values that exceed the specified range can not be correctly represented and are considered as _____

Answer (Please select your correct option)

☐ Overflow

correct

☐ Carry

☐ Parity

☐ Sign value

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 3 of 26

Marks: 1 (Budgeted Time 1 Min)

According to Demorgan's theorem:

$$\overline{A + B + C} = \underline{\hspace{2cm}}$$

Answer (Please select your correct option)

☐ A.B.C

☐ A + B.C

☒ $\overline{A} \overline{B} \overline{C}$

correct

☐ $\overline{A.B + C}$

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 4 of 26

Marks: 1 (Budgeted Time 1 Min)

If two numbers in BCD representation generate an invalid BCD number then the binary _____ is added to the result

Answer (Please select your correct option)

☐ 1001

☐ 0110

☐ 1111

☐ 1100

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 5 of 26

Marks: 1 (Budgeted Time 1 Min)

The output of an AND gate is one when _____

Answer (Please select your correct option)

☐ All of the inputs are one

correct



☐ Any of the input is one

☐ Any of the input is zero

☐ All the inputs are zero

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP & CALL: 03087122922

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 6 of 26

Marks: 1 (Budgeted Time 1 Min)

A standard SOP form has _____ terms that have all the variables in the domain of the expression.

Answer (Please select your correct option)

☐ Sum

☒ Product

correct



☐ Max

☐ Composite

MADE BY HADI

Email: hadiraiputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 7 of 26

Marks: 1 (Budgeted Time 1 Min)

A comparator circuit has multiple inputs and _____ outputs

Answer (Please select your correct option)

☐ 2

☐ 3

correct

☐ 4

☐ 7

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 8 of 26

Marks: 1 (Budgeted Time 1 Min)

An alternate method of implementing Comparators which allows the Comparators to be easily cascaded without the need for extra logic gates is _____

Answer (Please select your correct option)

- ☐ Using a single comparator
- ☐ Using Iterative Circuit based Comparators
- ☐ Connecting comparators in vertical hierarchy
- ☐ Extra logic gates are always required.

correct



MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 9 of 26

Marks: 1 (Budgeted Time 1 Min)

The active high and active low inputs of 3-to-8 Decoder are as follows:

Answer (Please select your correct option)

☐ One active-high and the remaining two are active-low.

correct



☐ Two active-high and the remaining one is active-low.

☐ All active high

☐ All active low

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 10 of 26

Marks: 1 (Budgeted Time 1 Min)

OLMC consists of a _____

Answer (Please select your correct option)

☐ Encoder

☐ Decoder

☐ Logic Gate

☐ Flip-Flop

correct

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 11 of 26

Marks: 1 (Budgeted Time 1 Min)

The Quad Multiplexer has _____ inputs

Answer (Please select your correct option)

☐ 4

☐ 8

☐ 12

☒ 16

correct



MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 12 of 26

Marks: 1 (Budgeted Time 1 Min)

The carry propagation can be expressed as _____.

Answer (Please select your correct option)

☐ $C_p = AB$

☐ $C_p = A + B$

☐ $C_p = A \oplus B$

☐ $C_p = A + \bar{B}$

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 13 of 26

Marks: 1 (Budgeted Time 1 Min)

In the binary number "1100.111", the first bit at the right of decimal point has the weight

Answer (Please select your correct option)

☐ $\frac{1}{2}$ (1 divided by 2)

☐ $\frac{1}{4}$ (1 divided by 4)

☐ 0

☐ 1


MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

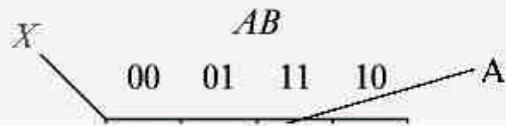Question No : 14 of 26

Marks: 1 (Budgeted Time 1 Min)

In the following Karnaugh map, which group has "legal grouping" ?



Answer (Please select your correct option)

A

☐

B

☐

C

☒

correct

D

☐

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 15 of 26

Marks: 1 (Budgeted Time 1 Min)

In CMOS 5 Volt series, Input voltage for Logic high signal (V_{IH}) is in the range of _____ volts.

Answer (Please select your correct option)

☐ 3.5 to 5

correct



☐ 4.5 to 5

☐ 0 to 5

☐ 0 to 3.5

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP & CALL: 03087122922

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 16 of 26

Marks: 1 (Budgeted Time 1 Min)

Programmable Array Logic (PAL) has _____ input(s) and _____ output(s).


Answer (Please select your correct option)

☐ Single, multiple

☐ Multiple, single

☐ Single, single

☒ Multiple, multiple

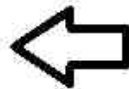

correct

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 17 of 26

Marks: 1 (Budgeted Time 1 Min)

An equivalent ABEL notation of Boolean expression $A+B$ is _____

Answer (Please select your correct option)

☐ A & B

☐ A I B

☒ A # B

☐ A \$ B



correct

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 18 of 26

Marks: 1 (Budgeted Time 1 Min)

Which circuit has the following Sum and CarryOut expressions?


$$\text{Sum} = A \oplus B \oplus C$$

$$\text{CarryOut} = C(A \oplus B) + AB$$

Answer (Please select your correct option)

☐ Half Adder

☒ Full Adder

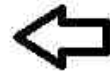

correct

☐ 3-bit parallel adder

☐ MSI adder circuit

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 19 of 26

Marks: 1 (Budgeted Time 1 Min)

From the truth table below, determine the standard SOP expression.

Inputs			Output
A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	0

Answer (Please select your correct option)

☐ $\overline{A}\overline{B}\overline{C} + \overline{A}BC + A\overline{B}\overline{C}$

☐ $AB\overline{C} + \overline{A}\overline{B}\overline{C} + \overline{A}BC$

correct

☐ $(A+B+\overline{C})(A+\overline{B}+\overline{C})(\overline{A}+\overline{B}+C)$

☐ $(\overline{A}+\overline{B}+C)(\overline{A}+B+C)+(A+B+\overline{C})$

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL-03087122922


MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

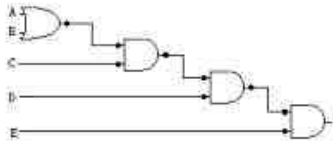Question No : 20 of 26

Marks: 1 (Budgeted Time 1 Min)

The Boolean expression for the logic circuit is _____



Answer (Please select your correct option)

☐ $AB+CDE$

☐ $(A+B)CDE$

correct

☐ $(A+B)+(CDE)$


☐ $(A+B)(CD+E)$

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 20 of 26

Marks: 1 (Budgeted Time 1 Min)

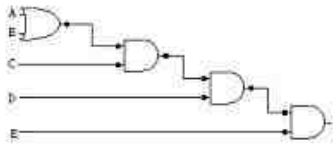

Answer (Please select your correct option)

☐ AB+CDE

☐ (A+B)CDE

☐ (A+B)+(CDE)

☐ (A+B)(CD+E)

correct



MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 21 of 26

Marks: 2 (Budgeted Time 4 Min)

How many possible outputs does a decoder of 3 inputs contain?

Answer ([Please click here to Add Answer](#))



MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question No : 22 of 26

Marks: 2 (Budgeted Time 4 Min)

Write down four uses of multiplexers.

Answer ([Please click here to Add Answer](#))



MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122922 (Team Hadi Lahore)

Answer (Please [click here](#) to Add Answer)




MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

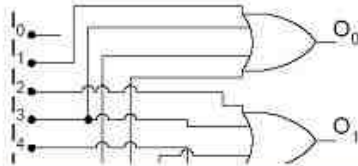Question No : 24 of 26

Marks: 3 (Budgeted Time 6 Min)

Identify the following circuit that is which combinational circuit is being represented by this diagram?



Answer (Please [click here](#) to Add Answer)



MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Map the following POS expression on a karnaugh map:

$$(\bar{A} + \bar{B} + C + D)(\bar{A} + B + \bar{C} + \bar{D})(A + B + \bar{C} + D)(\bar{A} + \bar{B} + \bar{C} + \bar{D})(A + B + \bar{C} + \bar{D})$$

Answer ([Please click here to Add Answer](#))




MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

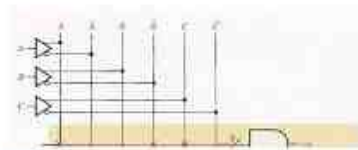Question No : 26 of 26

Marks: 5 (Budgeted Time 10 Min)

A programmed array is shown in Figure below. The intact fusible link, are indicated by small red Xs. Absence of an X means that the fuse is open. Analyze the figure below and write the output expression.



Answer ([Please click here to Add Answer](#))




MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question No : 26 of 26

Marks: 5 (Budgeted Time 10 Min)

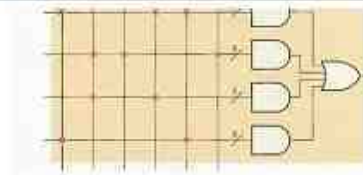

Answer ([Please click here to Add Answer](#))



MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

HADI VU PAST PAPER

WE DEAL ALL KIND OF VU PROJECT
(PHP, ANDROID, PYTHON)

DEAR STUDENTS

ARE YOU LOOKING
FOR ASSISTANCE

- 1) ASSIGNMENTS
- 2) QUIZZES
- 3) GDB
- 4) GRAND QUIZZES

We Provide, You Solution
of VU Academic Activities
include Assignments,
Quizzes, GDBs, Grand Quizzes
If You Need Help in Services
Kindly inform us.

TEAM HADI
(VU LAHORE)



TEAM HADI
(VU LAHORE)



HADI TECH

#PAID_TASK

CONTACT US

CALL & WHATSAPP

0308-7122922